

# Lab 1 discussion

Nicole Hamilton  
BEE 233 Fall 2015 Section AA

The whole point of Lab 1 is to familiarize you with the instruments.

# Resistors

You probably discovered resistance measurements are only good to about 3 digits.

Resistance goes up as they heat up, even with just the tiny current from the ohmmeter.

# My own results measuring 5 resistors

Resistor	Measured	% Error	Abs( % Error )
1	987	-1.30	1.30
2	975	-2.50	2.50
3	984	-1.60	1.60
4	982	-1.80	1.80
5	979	-2.10	2.10
Average	981	-1.86	1.86

They're supposed to be 5% resistors, so in this small sample, it looks like we got what we paid for.


# Power supplies at 5 V

Probably discovered that the Tek PS is slightly more accurate.

My own results:

	Setting	Displayed	Measured
Tek PWS 4205	5.000	5.001	5.0010
RSR HY3002-3		5.0	5.0287

# Current limit

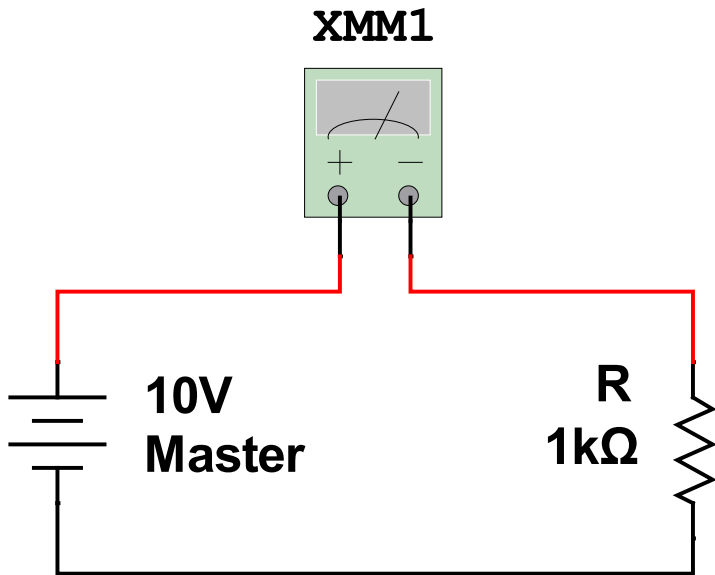


At max current, my results:

	Nominal	Measured
PS	10.0 V	10.069 V
R	1 KΩ	975 Ω
I	10 mA	10.35 mA
$I * R$	10.0 V	10.091 V

As the current knob was turned CCW, it hit a point where current and voltage began dropping quickly to about 1 mA and 1 V.

# Series mode

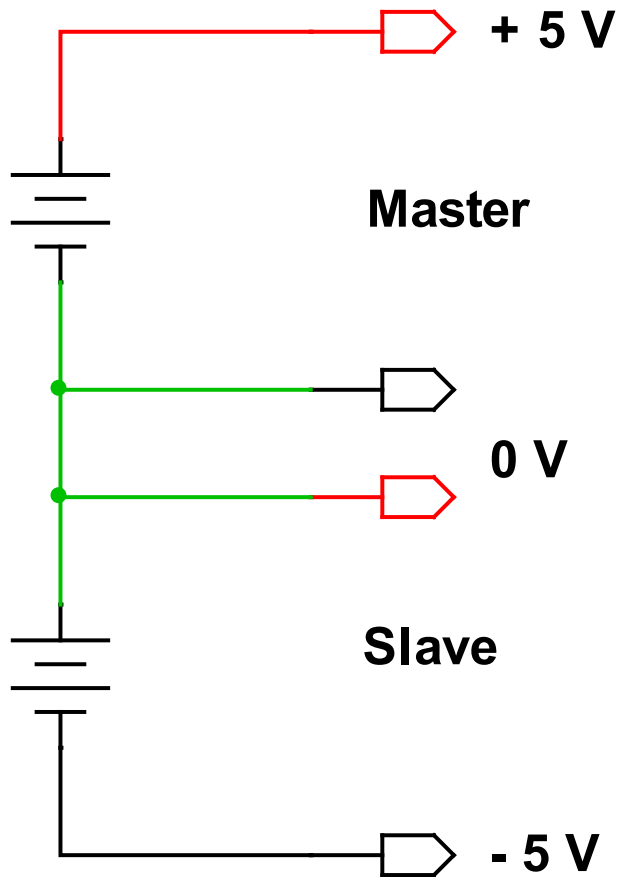

As you change the master, you change the slave.


# Function generator and oscilloscope

1. Sine wave 5.0 Vpp at 20 KHz with +1.0 V DC offset with measurements of Vpp, frequency and mean.
2. Pulse 2.0 Vpp at 100 Hz 80% duty cycle with measurements of Vpp and frequency and cursors to measure the duty cycle.

Hopefully, everyone was able to do this.



# Function generator output resistance

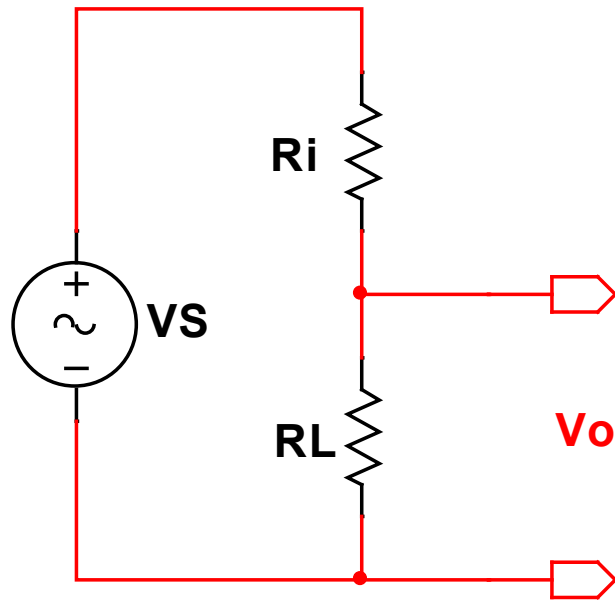

Function generator

Set for 400 Vpp @ 100 Hz


Either High Z or 50  $\Omega$  output

$R_L$  is either 51  $\Omega$  or 27 K $\Omega$

Four combinations


1. 50  $\Omega$  output and 51  $\Omega$  load
2. 50  $\Omega$  output and 27 K $\Omega$  load
3. High Z output and 51  $\Omega$  load
4. High Z output and 27 K $\Omega$  load

# 50 $\Omega$ output

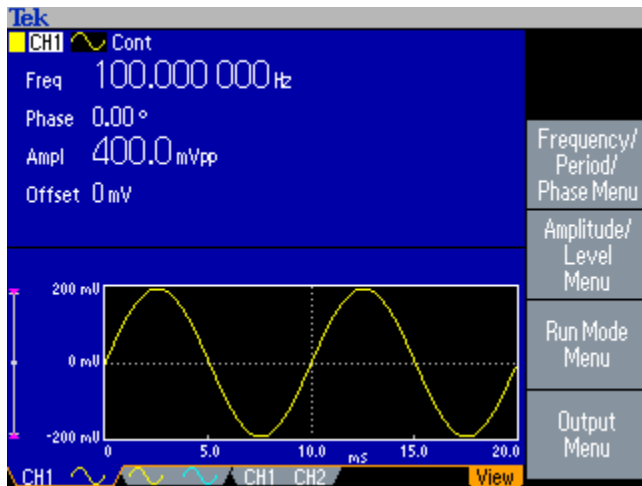


400 mVpp

100 Hz

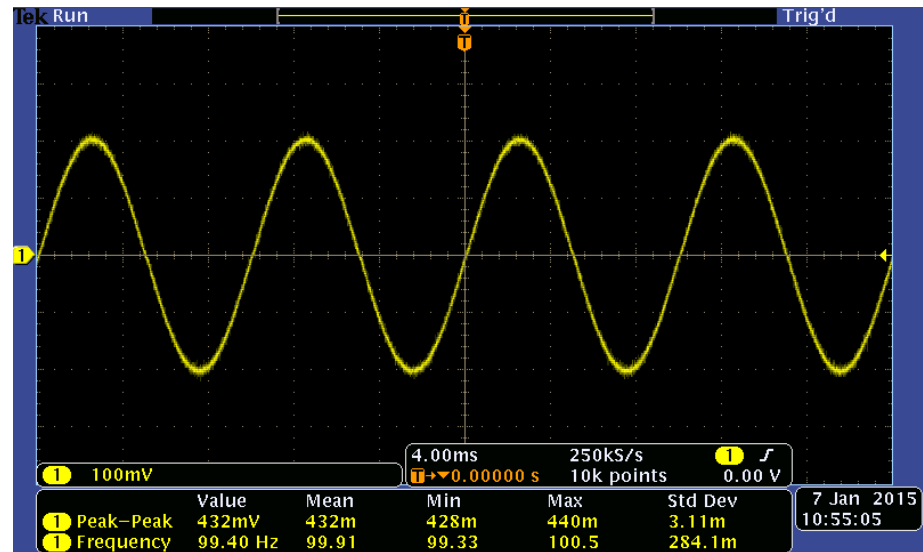


RL1 = 50.46  $\Omega$ , Vo1 = 432 mVpp

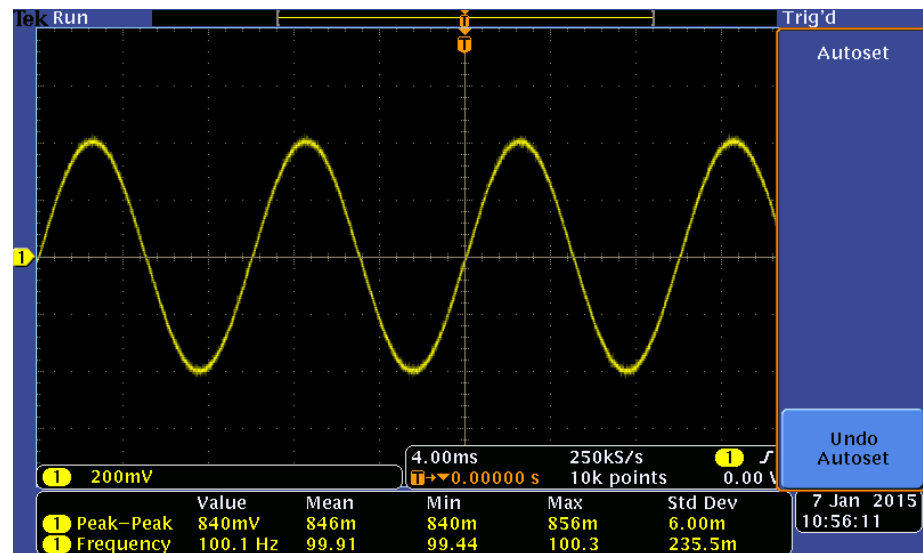


RL2 = 26.51 K $\Omega$ , Vo2 = 840 mVpp


# High Z output

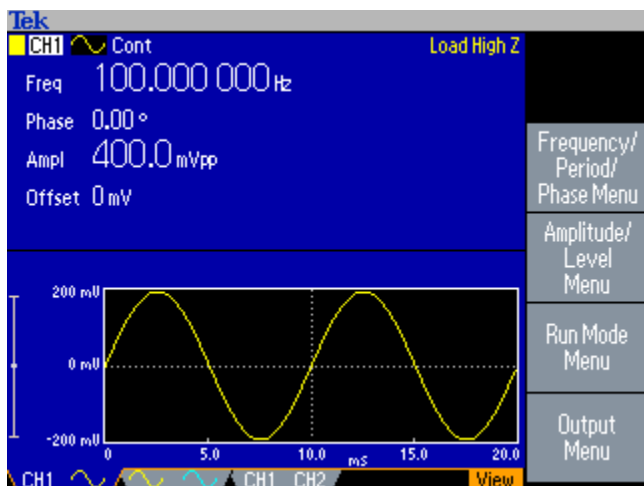


400 mVpp  
100 Hz

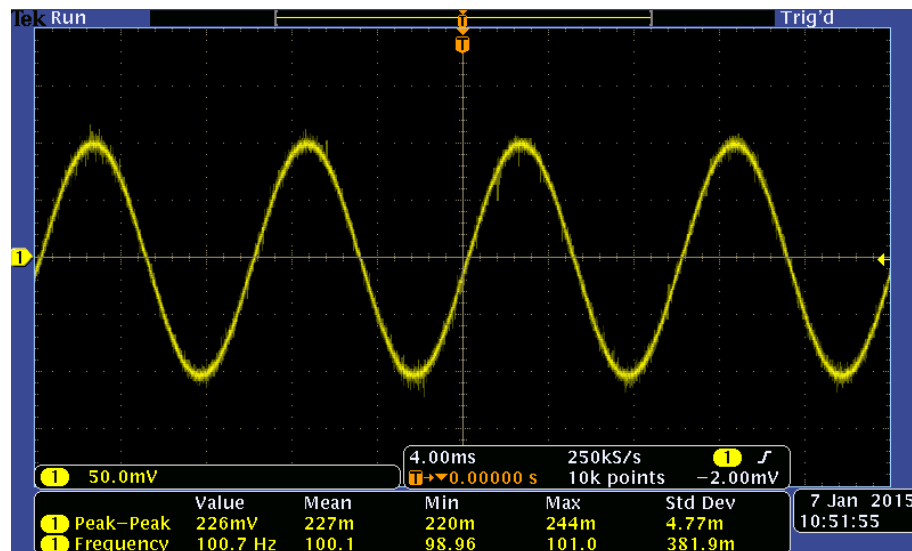

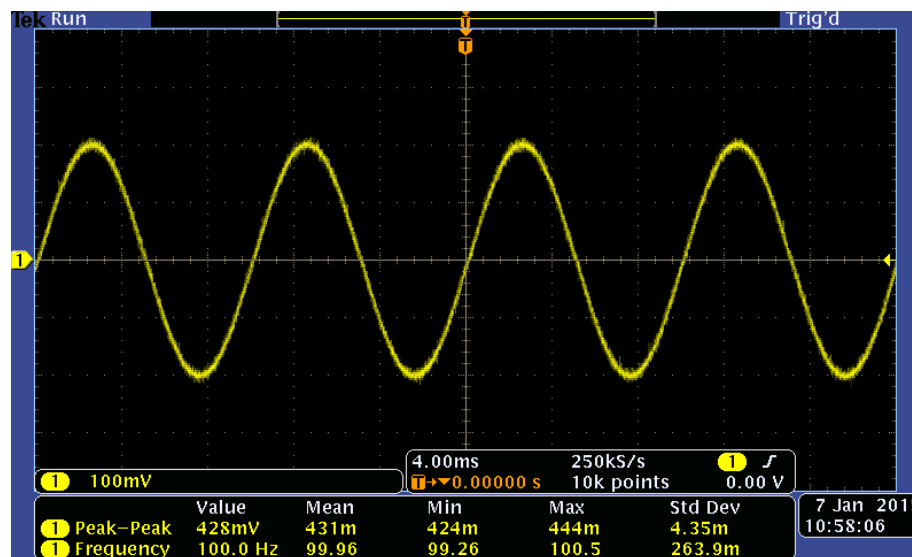$RL1 = 50.46 \Omega$ ,  $Vo1 = 227 \text{ mVpp}$




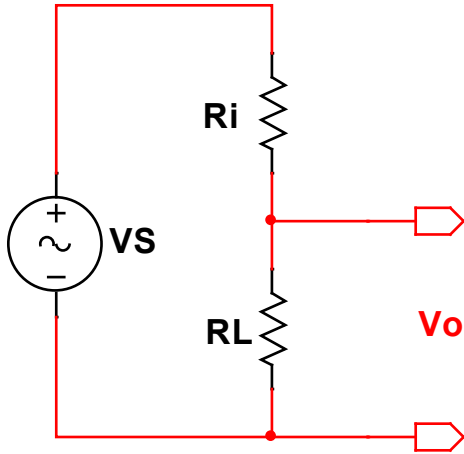$RL2 = 26.51 \text{ K}\Omega$ ,  $Vo2 = 431 \text{ mVpp}$


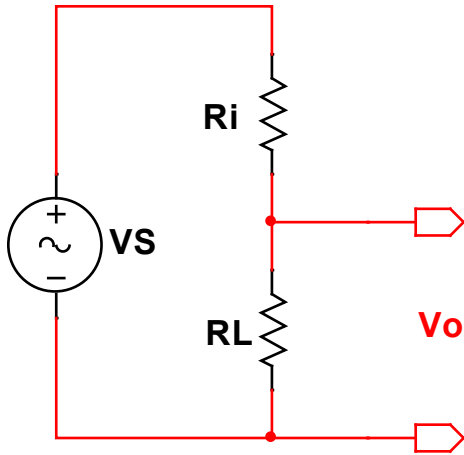
# Finding $R_i$

This is a bit of trick question because you don't actually have enough data.




## Finding $R_i$

Let's assume the function generator does indeed have something close to the claimed  $50\ \Omega$  output resistance.

With  $R_L = 27\ \text{K}\Omega$

$$V_o = \frac{27e3}{50 + 27e3} * V_S = .9982 * V_S$$

So let's approximate  $V_S \cong V_o$ .

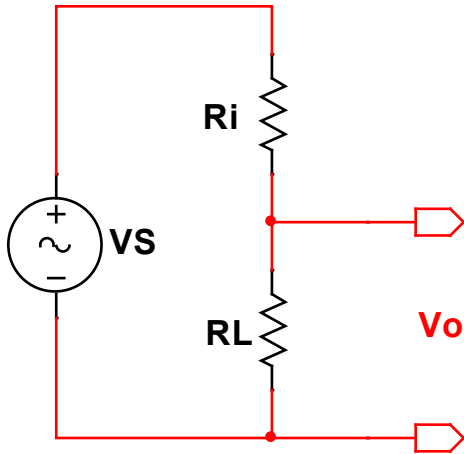

$$V_{o1} = \frac{RL1}{Ri + RL1} * VS$$

$$V_{o1} * (Ri + RL1) = RL1 * VS$$

$$V_{o1} * Ri + V_{o1} * RL1 = RL1 * VS$$


$$V_{o1} * Ri = RL1 * VS - V_{o1} * RL1$$

$$V_{o1} * Ri = RL1 * (VS - V_{o1})$$

$$Ri = \frac{RL1 * (VS - V_{o1})}{V_{o1}}$$

Assuming  $VS \cong V_{o2}$
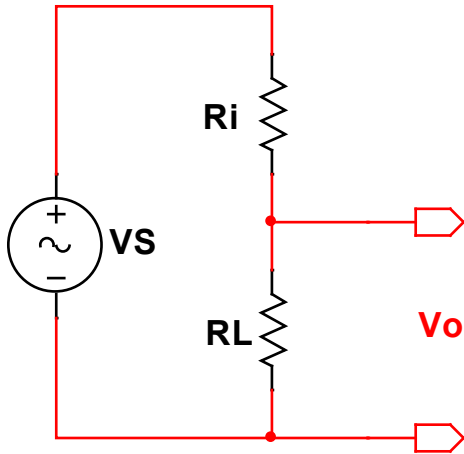
$$Ri = \frac{RL1 * (V_{o2} - V_{o1})}{V_{o1}}$$



$$R_i = \frac{R_{L1} * (V_{o2} - V_{o1})}{V_{o1}}$$

# My own results

$$R_{L1} = 50.46 \Omega$$

## For 50 $\Omega$ output

$$V_{o1} = 432 \text{ mVpp}$$

$$V_{o2} = 840 \text{ mVpp}$$

$$\text{Estimated } R_i = 47.7 \Omega$$

## For High Z output

$$V_{o1} = 227 \text{ mVpp}$$

$$V_{o2} = 431 \text{ mVpp}$$

$$\text{Estimated } R_i = 45.3 \Omega$$