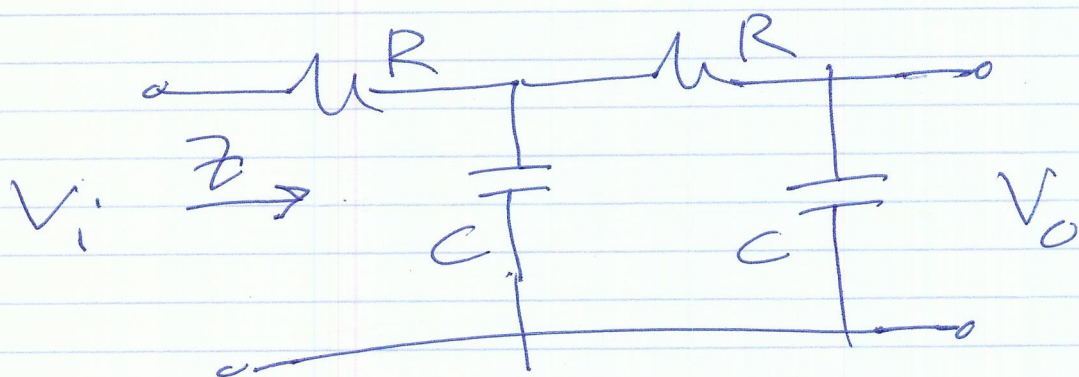


## Lab 2: Notes on the cascaded circuit Nicole Hamilton


The cascaded circuit is called a second-order circuit because it has 2 energy storage devices, i.e., 2 capacitors.



We expect the characteristic equation to be of the form

$$V_o = A_1 e^{s_1 t} + A_2 e^{s_2 t} + A_0$$

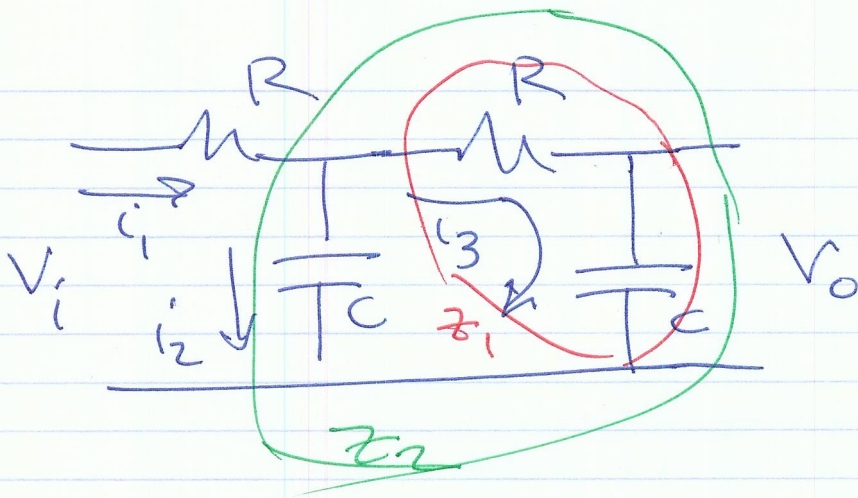To solve this, I'll write a polynomial equation for  $Z$  looking in, then find the roots where  $Z \rightarrow 0$  to determine the natural response, giving me  $s_1$  and  $s_2$ . I'll use initial and final conditions to determine the  $A_i$  values.



$$Z_1 = R + \frac{1}{sC}$$

$$Y_1 = \frac{1}{R + \frac{1}{sC}} = \frac{sC}{sRC + 1}$$

$$Y_2 = sC + Y_1 = sC + \frac{sC}{sRC + 1}$$

$$= \frac{s^2RC^2 + 2sC}{sRC + 1}$$

$$Z_2 = \frac{sRC + 1}{s^2RC^2 + 2sC}$$

$$Z = R + Z_2 = R + \frac{sRC + 1}{s^2RC^2 + 2sC}$$

$$Z = \frac{s^2R^2C^2 + 3sRC + 1}{sRC^2 + 2sC}$$

The natural response for this circuit will be given by the roots of the equation for  $Z$ , i.e., where  $Z \rightarrow 0$ .

$$Z = \frac{s^2 R^2 C^2 + 3sRC + 1}{sRC^2 + 2sC} = 0$$

$$s^2 R^2 C^2 + 3sRC + 1 = 0$$

$$s = \frac{-3RC \pm \sqrt{9R^2 C^2 - 4R^2 C^2}}{2R^2 C^2}$$

For  $R = 10k$  and  $C = 0.01 \mu F$

$$s_1 = -3,819.66 \text{ radians/sec}$$

$$s_2 = -26,180.34 \text{ radians/sec}$$

$$V_0 = A_1 e^{s_1 t} + A_2 e^{s_2 t} + A_0$$

We now know  $s_1$  and  $s_2$ ,

$A_0$  is given by inspection

that as  $t \rightarrow \infty$ ,  $V_0 \rightarrow V_i$

$$\therefore A_0 = V_i$$

To find  $A_1$  and  $A_2$  we need to consider the initial conditions for  $V_0$  and  $dV_0/dt$  at  $t = 0^+$ .

$V_0|_{0^+} = 0$  because both capacitors are uncharged


$$\therefore A_1 + A_2 + V_i = 0$$

$$A_2 = -(A_1 + V_i)$$

$$\frac{dV_0}{dt} = A_1 s_1 e^{s_1 t} + A_2 s_2 e^{s_2 t}$$

$$\left. \frac{dV_0}{dt} \right|_{0^+} \text{ must} = \left. i_2 C \right|_{0^+}$$

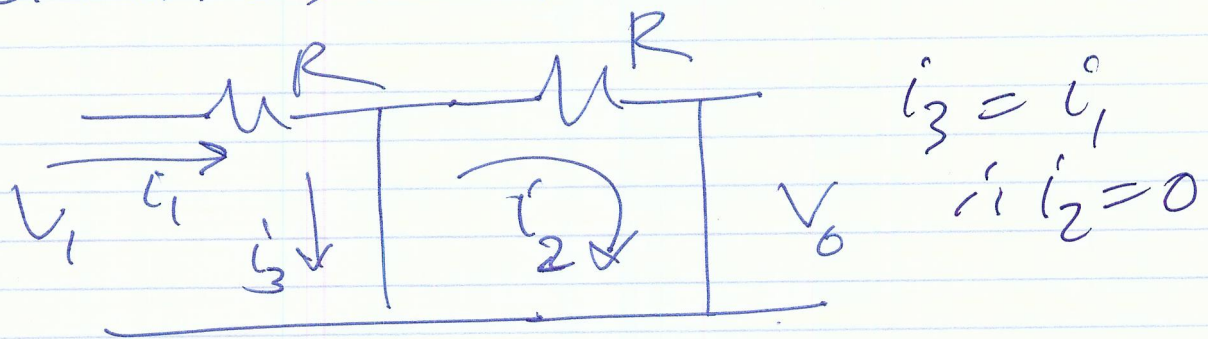At  $t=0+$ ,  $i_2$  must be zero because with both capacitors discharged, they look like shorts;



$$\left. \frac{dV_o}{dt} \right|_{0+} = A_1 s_1 + A_2 s_2 = i_2 C \Big|_{0+} = 0$$

Substituting  $A_2 = -(A_1 + V_i)$

$$A_1 s_1 - (A_1 + V_i) s_2 = 0$$

$$A_1 s_1 - A_1 s_2 - V_i s_2 = 0$$

$$A_1 (s_1 - s_2) = V_i s_2$$

$$A_1 = V_i \frac{s_2}{s_1 - s_2}$$

$$A_2 = - \left( V_i \frac{s_2}{s_1 - s_2} + V_i \right)$$

$$= -V_i \left( \frac{s_2}{s_1 - s_2} + 1 \right)$$

We now have the complete characteristic equation

$$V_o = A_1 e^{s_1 t} + A_2 e^{s_2 t} + A_0$$

$$A_0 = V_i$$

$$s_1 = -3819.66$$

$$s_2 = -26,180.34$$

$$A_1 = V_i \left( \frac{s_2}{s_1 - s_2} \right) = -1.171 V_i$$


$$A_2 = -V_i \left( \frac{s_2}{s_1 - s_2} + 1 \right) = 0.171 V_i$$

$$\frac{V_o}{V_i} = -1.171 e^{-3819.66t} + 0.171 e^{-26180.34t} + 1$$

To find  $t_{PUH}$ , I solved numerically for  $\frac{V_o}{V_i} = 0.5$ .

$$t_{PUH} = 222.49 \mu s$$

Here was my simulation.

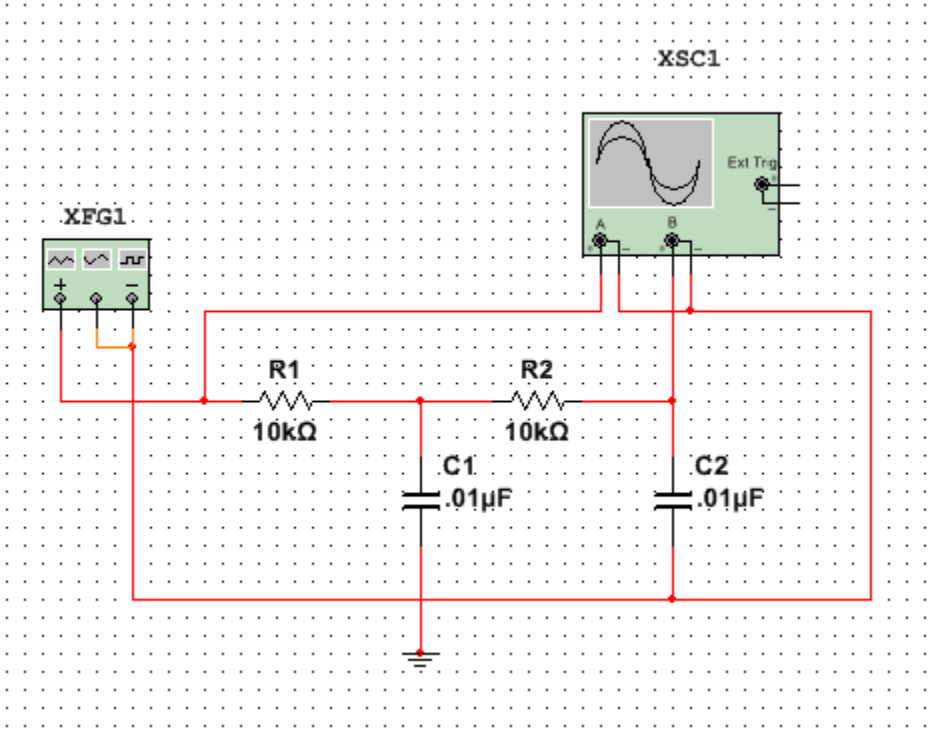


My calculated value for  $t_{PLH}$  matches exactly with the granularity of the simulation, seen on the next page.

	Calculated	Simulated
$t_{PLH}$	222.49 $\mu$ s	Between 217.803 and 227.273 $\mu$ s

Here is a comparison of the calculated delay times for the simple (from the prelab) and cascaded circuits.

	Simple	Cascaded	Ratio
$t_{PLH}$	69.31 $\mu$ s	222.49 $\mu$ s	3.21

$t_{PLH} > 217.803 \mu s$

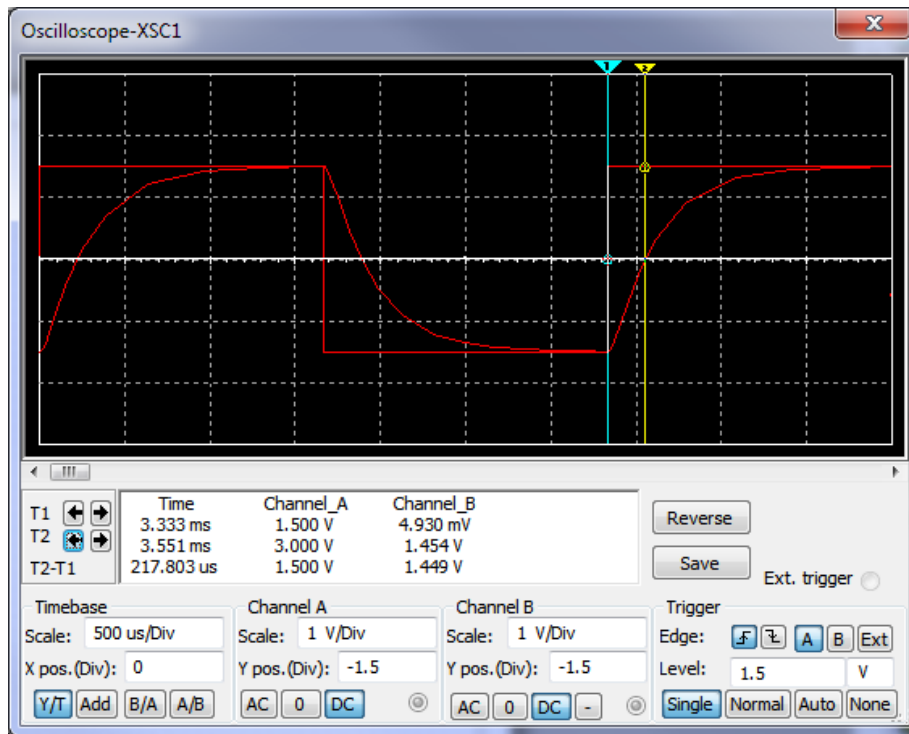

$t_{PLH} < 227.273 \mu s$

