

BEE 233 Circuits
Fall 2015
Lab 4: Opamp filters prelab notes

1 Circuits

You'll be analyzing these five opamp circuits in this lab. In all cases, the opamp is the same LM348 you worked with in Lab 3, $V_{CC} = +12\text{ V}$ and $V_{EE} = -12\text{ V}$.

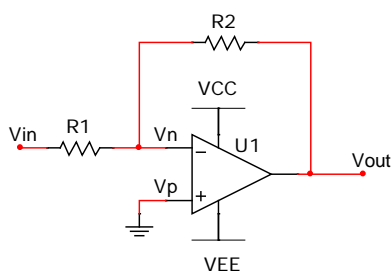


Figure 1. Inverting amplifier.

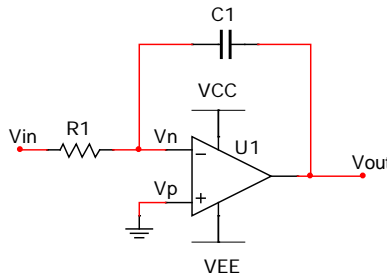


Figure 2. Simple integrator.

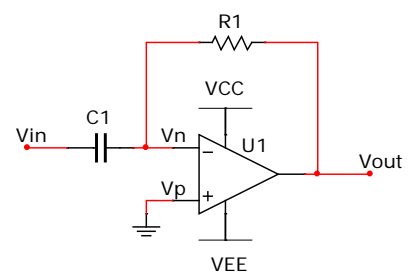


Figure 3. Simple differentiator.

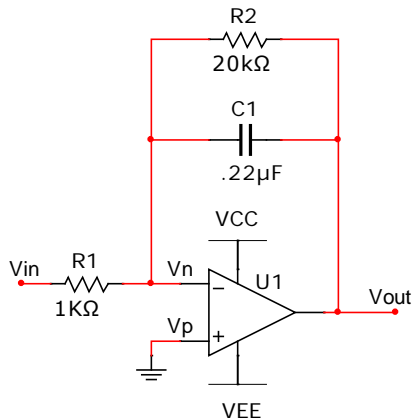


Figure 4. Integrator with shunt.

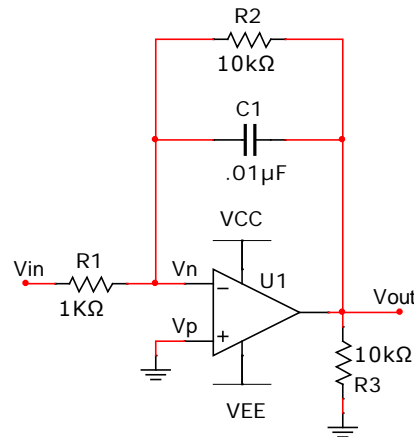


Figure 5. Low-pass filter.

4 Inverting amplifier

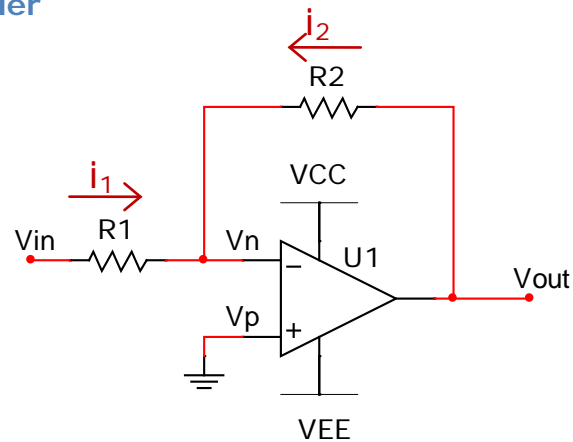


Figure 12. Inverting amplifier.

1. Analyze the inverting amplifier circuit in figure 12 (same as figure 1) to derive an equation for the gain, A_v , as a function of R_1 and R_2 .

$$V_n = V_p = 0$$

$$i_1 = -i_2$$

$$V_{in} = i_1 R_1 + V_n = i_1 R_1$$


$$V_{out} = i_2 R_2 + V_n = i_2 R_2 = -i_1 R_2$$

$$A_v = \frac{V_{out}}{V_{in}} = -\frac{i_1 R_2}{i_1 R_1} = -\frac{R_2}{R_1}$$


2. Choose values for R_1 and R_2 to produce a gain, $A_v = -10$.

$$\text{For } A_v = -10 \text{ and } R_1 = 1 \text{ k}\Omega, R_2 = 10 \text{ k}\Omega$$

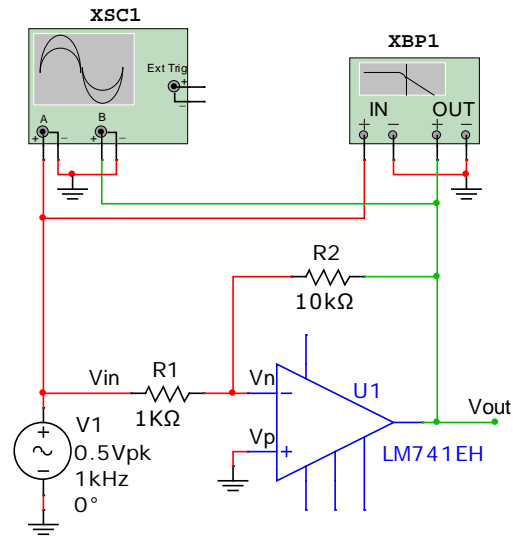
3. Simulate your circuit. Capture images of the following.
 - a. Your schematic.



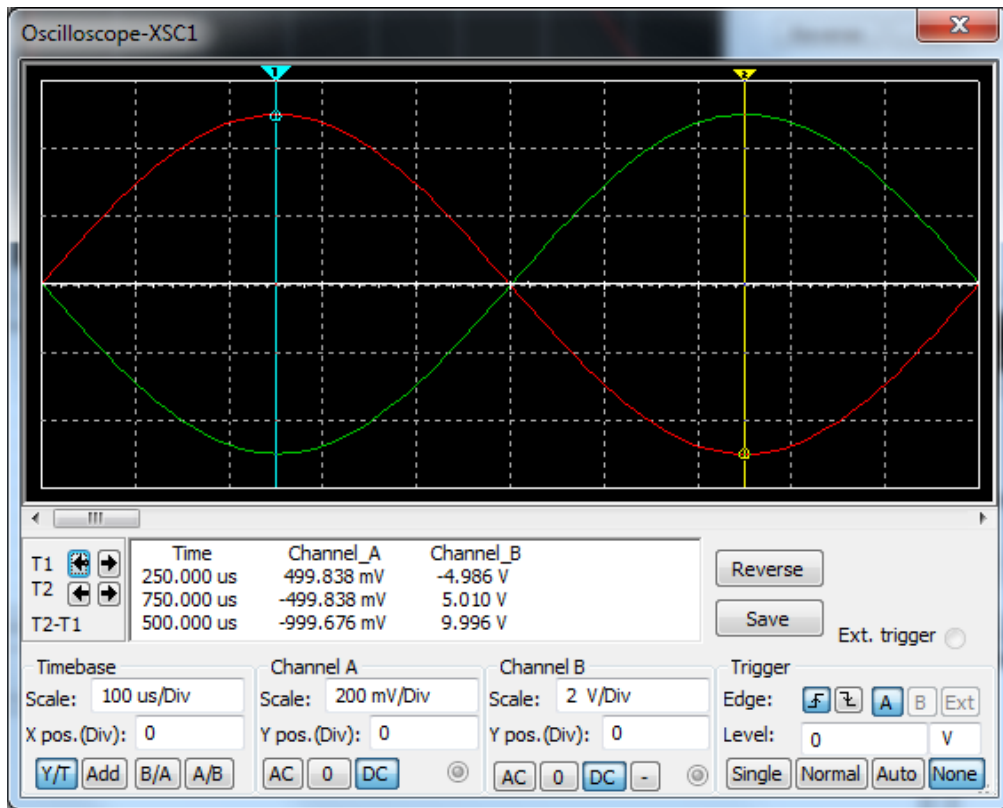- b. An oscilloscope display of V_{in} and V_{out} for $V_{in} = 1.0$ Vpp, 1 KHz sine wave, 0 V DC offset.



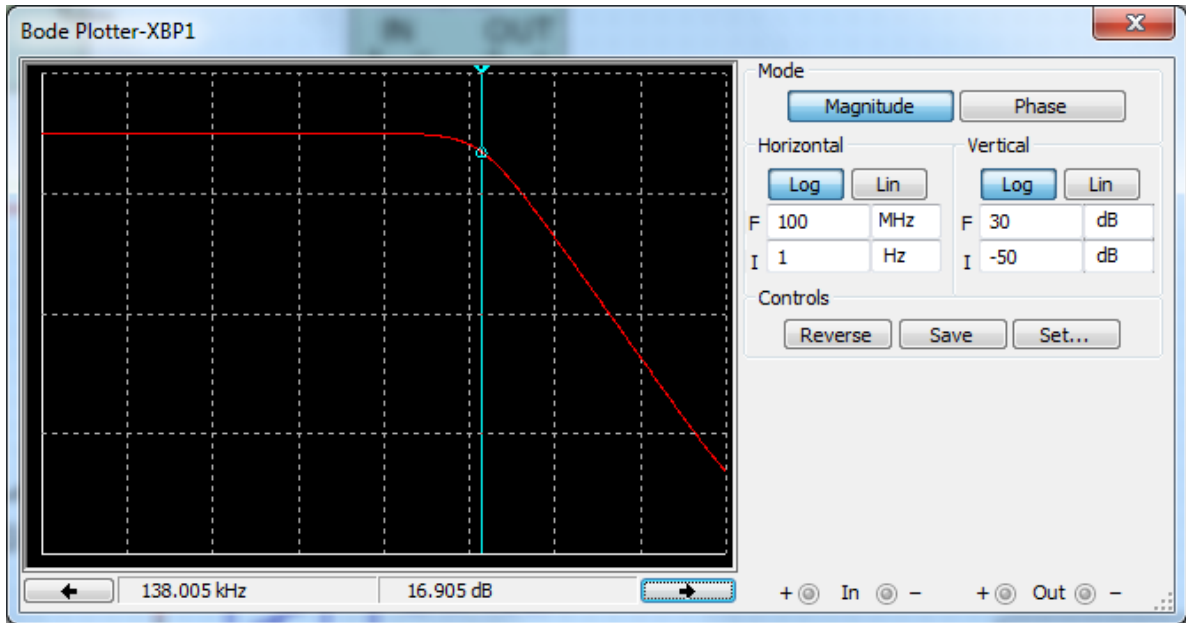- c. A Bode plot of the frequency response with a cursor at the cutoff frequency.



Cutoff is at about 138 KHz.

5 Simple integrator

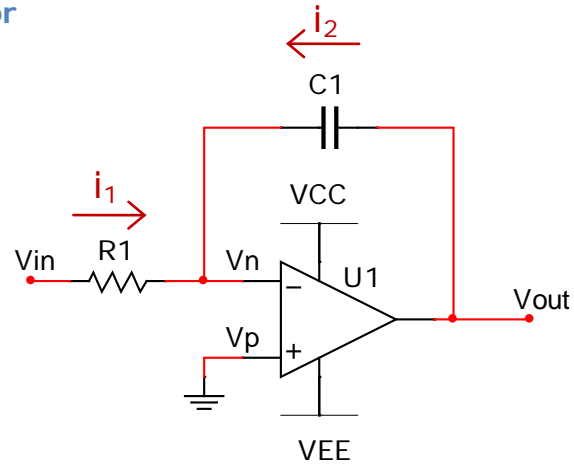


Figure 13. Simple integrator.

1. Analyze the integrator circuit in figure 13 (same as figure 2) to derive an equation for $V_{out}(t)$ as a function of $V_{in}(t)$. Show that the output is the integral of the input.

$$V_{in} = i_1 R_1$$

$$i_1 = \frac{V_{in}}{R_1} = -i_2$$

$$V_{out} = \int_0^t \frac{i_2}{C_1} dt$$

$$V_{out} = - \int_0^t \frac{V_{in}}{R_1 C_1} dt = - \frac{1}{R_1 C_1} \int_0^t V_{in} dt$$

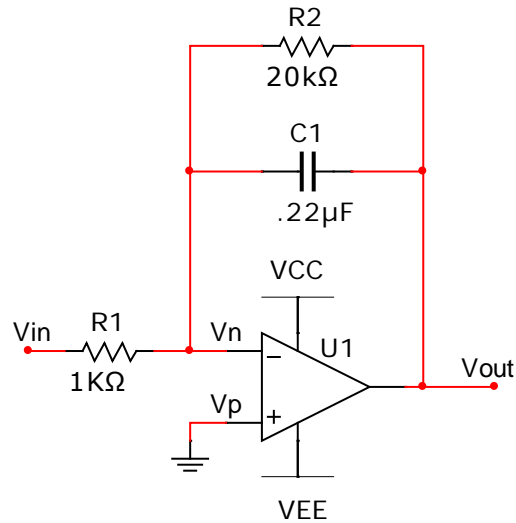


Figure 14. Integrator with shunt.

- Analyze the circuit in figure 14 (same as figure 4) to calculate the low-frequency gain.

Show that for $\gg \frac{1}{R_2 C_1}$, this circuit also functions as integrator.

At low frequency $Z_{C1} \rightarrow \infty$, making it behave like the inverting amp in 6.1.

$$A_v = -\frac{R_2}{R_1} = -\frac{20 \text{ K}\Omega}{1 \text{ K}\Omega} = -20$$

At high frequency, the impedance of the capacitor is much less than that of R_2 , making it behave like an integrator.

$$Z_{C1} = \frac{1}{sC_1} \ll R_2$$

- Simulate this circuit and capture images of your schematic and of oscilloscope displays of V_{in} and V_{out} with V_{in} set to be a sine wave, a square wave and a triangle wave. In each case, set $V_{in} = 1.0 \text{ Vpp}$ at 1 KHz, 0 V DC offset.
- Build this circuit and capture screenshots with V_{in} set to be a sine wave, a square wave and a triangle wave = 1.0 Vpp at 1 KHz, 0 V DC offset.
- Reset $V_{in} = 0.5 \text{ Vpp}$ sine wave at 1 KHz, 0 V DC offset. While it's running, watch the oscilloscope as you remove R_2 and then put it back. Describe what you observed. What is the purpose of R_2 ?

6 Simple differentiator

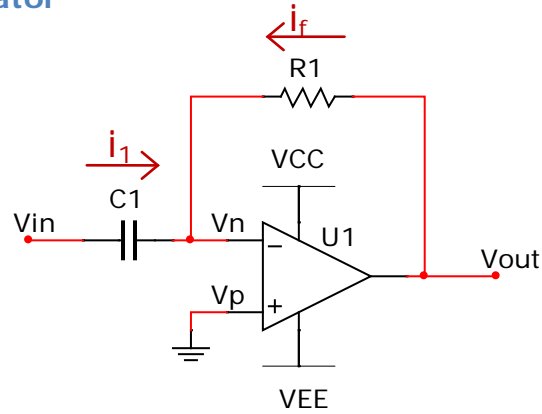


Figure 15. Simple differentiator.

1. Analyze the differentiator circuit in figure 15 (same as figure 3) to derive an equation for $V_{out}(t)$ as a function of $V_{in}(t)$. Show that the output is the derivative of the input.

$$V_{out} = i_f R_1$$

$$i_f = \frac{V_{out}}{R_1} = -i_1$$

$$V_{in} = \int_0^t \frac{i_2}{C_1} dt$$

$$V_{in} C_1 = \int_0^t i_2 dt$$

$$i_2 = C_1 \frac{dV_{in}}{dt}$$

$$i_2 = C_1 \frac{dV_{in}}{dt} = -\frac{V_{out}}{R_1}$$

$$V_{out} = -R_1 C_1 \frac{dV_{in}}{dt}$$

2. Simulate or build the circuit with $R1 = 1\text{ K}\Omega$ and $C1 = 0.22\ \mu\text{F}$ and capture screenshots with $V_{in} = 1.0\text{ Vpp}$ sine, triangle and square wave at 1 KHz. Describe what you observe. Does the circuit work as you expected? Can you explain the behavior?

7 Low pass filter

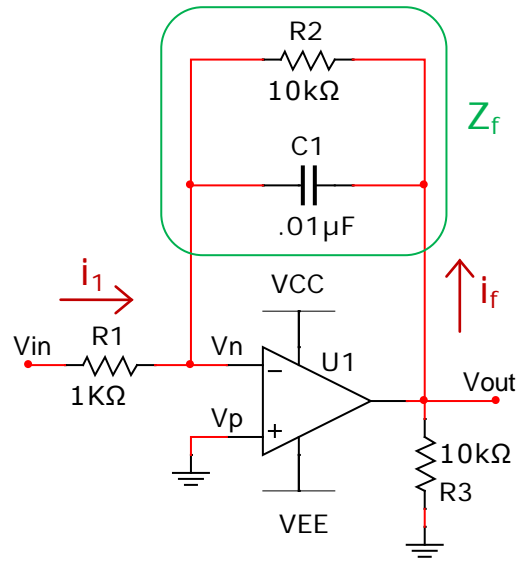


Figure 16. Low-pass filter.

1. Analyze the low-pass filter circuit in figure 16 (same as figure 5) to show that for $V_{in}(t) = A\cos(\omega t)$:

$$V_{out}(t) = -\frac{R_2}{R_1} A\cos(\omega t) \left(\frac{1 - j\omega R_2 C_1}{1 + \omega^2 R_2^2 C_1^2} \right)$$

$$Y_f = \frac{1}{R_2} + sC_1$$

$$Z_f = \frac{1}{Y_f} = \frac{1}{\frac{1}{R_2} + sC_1} = \frac{R_2}{sR_2C_1 + 1}$$

$$i_f = \frac{V_{out}}{Z_f} = V_{out} \left(\frac{sR_2C_1 + 1}{R_2} \right)$$

$$i_1 = \frac{V_{in}}{R_1}$$

$$i_f = -i_1$$

$$\frac{V_{in}}{R_1} = -V_{out} \left(\frac{sR_2C_1 + 1}{R_2} \right)$$

$$\frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1} \left(\frac{1}{sR_2C_1 + 1} \right)$$

$$V_{in} = A \cos(\omega t)$$

$$s = j\omega$$

$$\frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1} \left(\frac{1}{j\omega R_2 C_1 + 1} \right)$$

$$\left(\frac{1}{j\omega R_2 C_1 + 1} \right) \left(\frac{1 - j\omega R_2 C_1}{1 - j\omega R_2 C_1} \right) = \left(\frac{1 - j\omega R_2 C_1}{1 + R_2^2 C_1^2} \right)$$

$$\frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1} \left(\frac{1 - j\omega R_2 C_1}{1 + \omega^2 R_2^2 C_1^2} \right)$$

$$G = \frac{|V_{out}|}{|V_{in}|} = \frac{R_2}{R_1} \left| \frac{1 - j\omega R_2 C_1}{1 + \omega^2 R_2^2 C_1^2} \right|$$

$$R_1 = 1K = 10^3$$

$$R_2 = R_3 = 10K = 10^4$$

$$C_1 = 0.01 \mu F = 10^{-8}$$

$$G = \frac{R_2}{R_1} \left| \frac{1 - j\omega(10^4)(10^{-8})}{1 + \omega^2(10^4)^2(10^{-8})^2} \right| = \frac{R_2}{R_1} \left| \frac{1 - j\omega(10^{-4})}{1 + \omega^2(10^{-8})} \right|$$

$$G = \frac{R_2}{R_1} \left(\frac{1}{1 + \omega^2(10^{-8})} \right) |1 - j\omega(10^{-4})|$$

$$|1 - j\omega(10^{-4})| = \sqrt{1 + \omega^2(10^{-8})}$$

$$G = \frac{R_2}{R_1} \left(\frac{1}{1 + \omega^2(10^{-8})} \right) \sqrt{1 + \omega^2(10^{-8})}$$

$$G = \frac{R_2}{R_1} \left(\frac{1}{\sqrt{1 + \omega^2(10^{-8})}} \right)$$

$$G = \frac{R_2}{R_1} \left(\frac{1}{\sqrt{1 + \omega^2(10^{-8})}} \right) \left(\frac{10^4}{10^4} \right) = \frac{R_2}{R_1} \left(\frac{10^4}{\sqrt{10^8 + \omega^2}} \right)$$

2. Show that for the component values shown, the voltage gain, A_v , of this circuit is:

$$A_v = \frac{V_{out}}{V_{in}} = -\frac{10^5}{\sqrt{10^8 + \omega^2}}$$

3. Create a Bode plot of the expected gain from 1 Hz to 100 KHz and calculate the expected cutoff frequency.
4. Simulate your circuit. Capture images of the following.
 - a. Your schematic.
 - b. An oscilloscope display of V_{in} and V_{out} for $V_{in} = 1.0$ Vpp, 1 KHz sine wave, 0 V DC offset.
 - c. A Bode plot of the frequency response with a cursor at the 3 dB point.
5. Breadboard the circuit and capture screenshots with $V_{in} = 1.0$ Vpp sine wave, 0 V DC offset, at 100 Hz, 1 KHz and 10 KHz.
6. Find the frequency at which gain has dropped by 3 dB and capture a screenshot.
7. Create a table of measurements at increasing frequencies from 100 Hz to 100 KHz in a 1-2-5-10 sequence. Try to hold V_{in} fairly constant as you increase the frequency.

Frequency (Hz)	V_{in}	V_{out}	Gain (A_v)	Gain (dB)
100				
200				
500				
1K				
2K				
:				
50K				
100K				

8. Create a Bode plot of Gain(dB) versus frequency from your measurements.
9. Compare your three Bode plots and cutoff frequencies based on your calculations, your simulation and your experimental results and explain any differences.