

# BEE 271 Digital circuits and systems

Spring 2017

Lecture 1: Orientation and intro to logic circuits

Nicole Hamilton

<https://faculty.washington.edu/kd1uj>



## Nicole Hamilton

<https://faculty.washington.edu/kd1uj/>  
[kd1uj@uw.edu](mailto:kd1uj@uw.edu)

H: 425-702-8184

C: 425-765-9574

Office hours by appointment  
(I do not have an on-campus office.)

## Education

BS & MS EE, Stanford, 1973.

MBA, Boston University, 1987.

## Background

Most of it as an entrepreneur selling a C shell I wrote for Windows.

Also worked at IBM, Microsoft and RealNetworks.

At Microsoft, I wrote the ranker and query language for the first release of what's now Bing.

Here at UWB since 2013, initially as a Capstone advisor.

W Hamilton C shell - Wikipe... x

← → ↻ [https://en.wikipedia.org/wiki/Hamilton\\_C\\_shell](https://en.wikipedia.org/wiki/Hamilton_C_shell) ☆ ABP ⓧ ⏪ H ⏩ ☰

Msnicki 0 0 Talk Sandbox Preferences Beta Watchlist Contributions Log out

Article Talk Read Edit View history ⭐ More TW Search

**WIKIPEDIA**  
The Free Encyclopedia

Main page  
Contents  
Featured content  
Current events  
Random article  
Donate to Wikipedia  
Wikipedia store

Interaction  
Help  
About Wikipedia  
Community portal  
Recent changes  
Contact page

Tools  
What links here  
Related changes  
Upload file  
Special pages  
Permanent link  
Page information

# Hamilton C shell

From Wikipedia, the free encyclopedia

**Hamilton C shell** is a clone of the Unix C shell and utilities<sup>[1][2]</sup> for Microsoft Windows created by Nicole Hamilton<sup>[3]</sup> at Hamilton Laboratories as a completely original work, not based on any prior code. It was first released on OS/2 on December 12, 1988<sup>[4][5][6][7][8][9]</sup> and on Windows NT in July 1992.<sup>[10][11][12]</sup> The OS/2 version was discontinued in 2003 but the Windows version continues to be actively supported.

**Contents** [hide]

- Design
  - Parser
  - Threads
  - Windows conventions
- References
- External links

## Hamilton C shell



64-bit Hamilton C shell on a Windows 7 desktop.

**Original author(s)** Nicole Hamilton

**Initial release** December 12, 1988; 27 years ago

**Stable release** 5.2 / September 15, 2014; 20 months ago

**Written in** C

**Operating system** Windows

**Type** Unix Shell on Windows

Download a free copy from my faculty page.

This is my sixth time teaching this class.  
I hope to improve each time.  
I do pay attention to my student evaluations.

## **Lectures**

Mondays and Wednesdays

5:45 pm to 7:45 pm

Beardslee 260

## **Labs**

Mondays

3:30 pm to 5:30 pm


Beardslee 220

# Topics

1. Combinatorial logic.
2. Synchronous sequential logic and finite state machines.
3. Verilog and FPGAs.


# Combinatorial vs. Sequential Logic
 
## *Combinatorial or combinational logic*



1. No memory elements.
2. No feedback from the outputs to the inputs.
3. Outputs depend only on the inputs.

## *Sequential logic*

 

1. Contains memory that can remember a present state.
2. Outputs feed back to the inputs.
3. Outputs depend on both inputs and the present state.

# Will not cover

1. Asynchronous (non-clocked) logic.
2. Processor architecture, pipelining, etc.





# Grading


Homework	10%
Labs	30%
Midterm	30%
Final	30%

You may do both labs and homework in pairs.


I grade on the curve. I expect most grades should fall between 2.7 and 4.0 with a mean around 3.3 to 3.4, then fit the results.

  Most people do well on homework and labs, so most of the difference between a 4.0 and a 2.7 is performance on the exams.



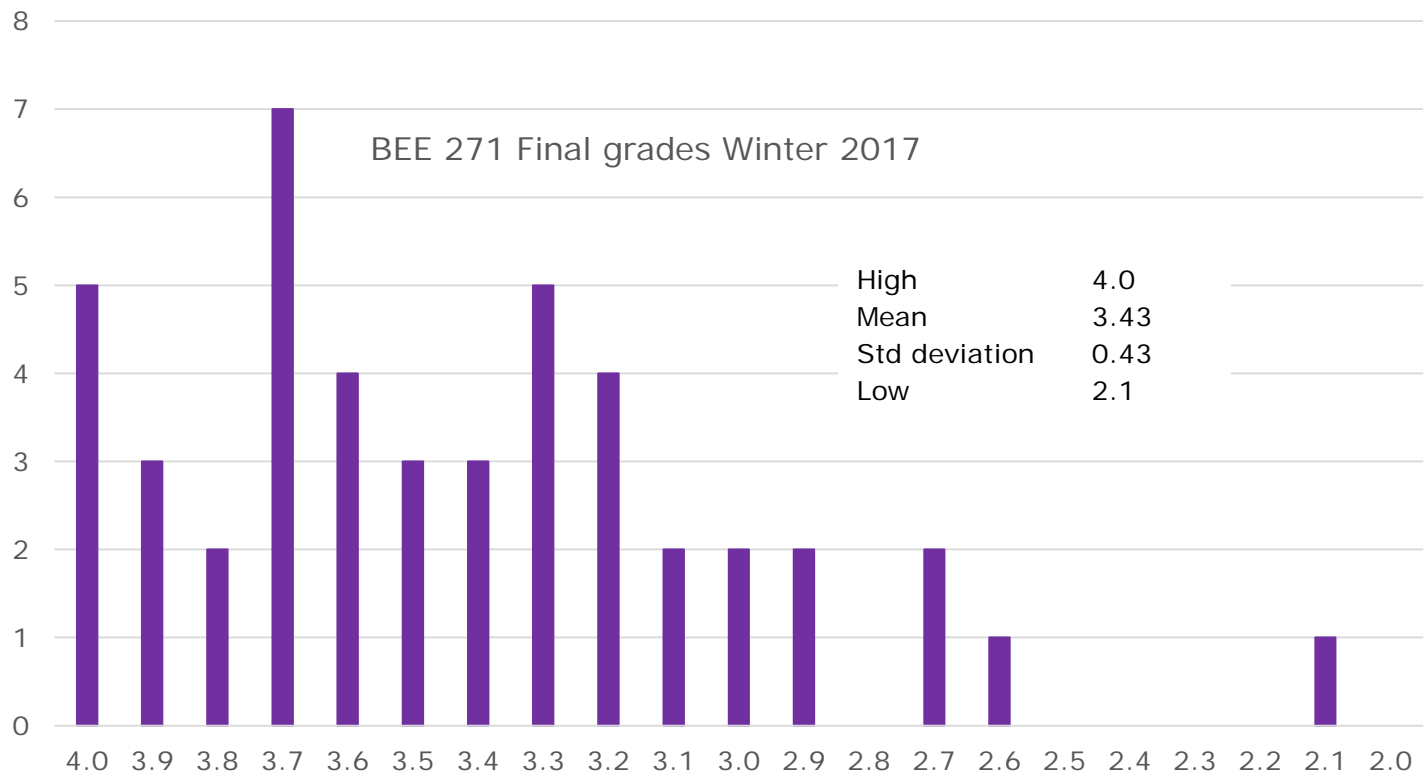

# Required text

 

*Fundamentals of Digital Logic with  
Verilog Design, Third Edition*


Stephen Brown

Zvonko Vranesic

McGraw-Hill Education, 2013

ISBN 978-0073380544

# Required text

 

We will cover chapters 1 through 6 plus section 9.2 on hazards.


You will also need to read Appendix A, a tutorial on Verilog.

# All the work must be your own

1. Copying answers from another student or off the internet will get a zero, even if you're clear about where you got them.
2. If you omit the attribution, submit work that's not your own or try to deceive me with fabricated results, you will, in addition, find yourself reported for academic misconduct.
3. I'm good at spotting misconduct and very good at reporting it.
4. ***I do not give warnings. I report everything.***

# Fundamentals of Digital Logic

## Chapter 1. Introduction

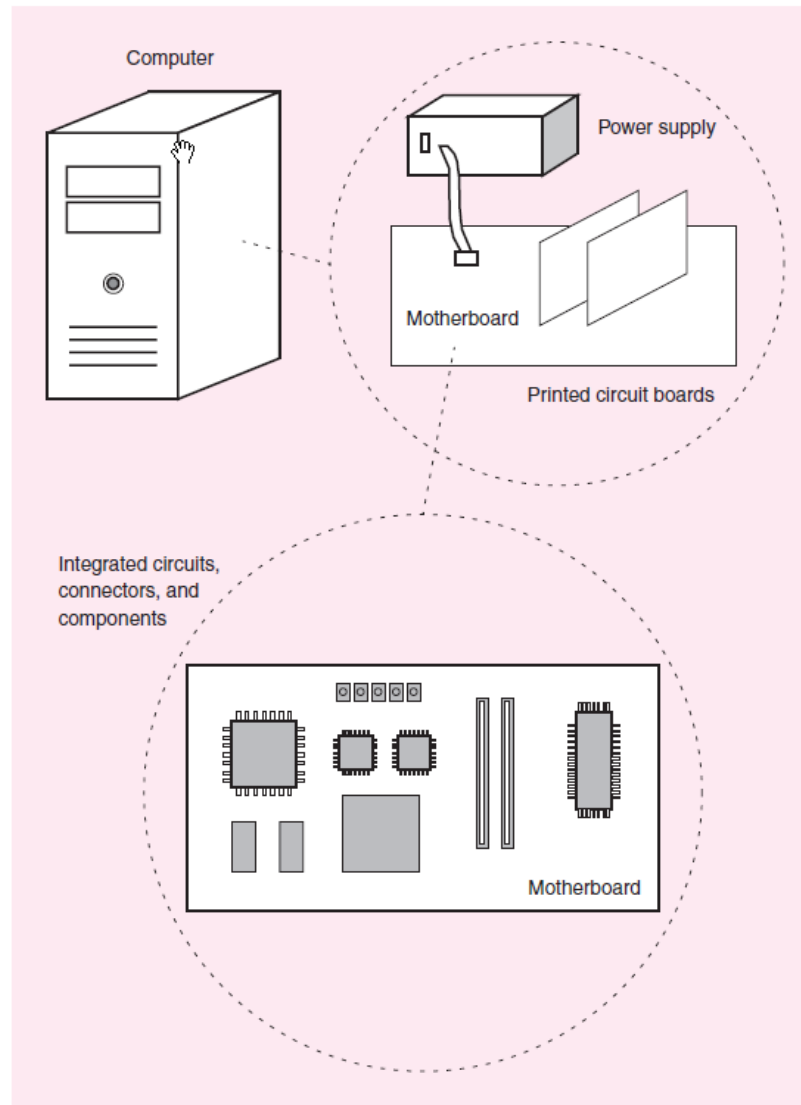

**Figure 1.4** A digital hardware system (Part a).



Focus of this course

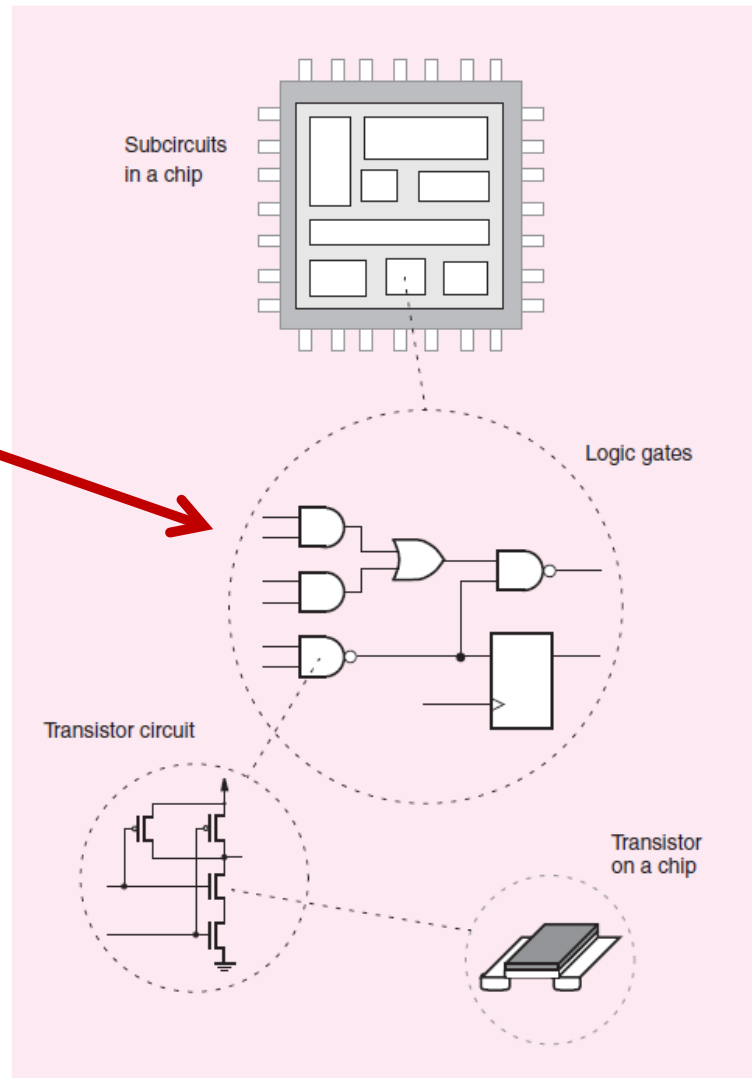
 


Figure 1.4 A digital hardware system (Part b).

# Digital hardware devices

## **Standard chips**

7400 series transistor-transistor logic (TTL) small scale integration (SSI) parts.

## **Field programmable logic devices (FPGAs)**

Programmed with Verilog or VHDL hardware programming languages or by dragging and dropping logic gates onto a schematic to do anything you want.

Downsides: Volatile and slow.


## **Application-specific integrated circuits (ASICs)**

Custom or semi-custom depending on the volume.


Hugely expensive.

Allows a single chip to be used, conserving board space and making a tiny final product possible.


# Four labs to support the lectures.

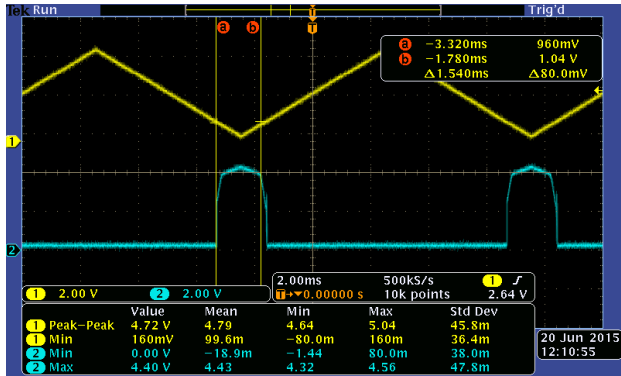


1. Digital logic devices.

 

2. Hex adding machine.

 


3. Keypad scanner.

 

4. Keypad debouncer.

# Terasic DE1-SoC

 

\$175 academic price

## FPGA

- Altera Cyclone V SoC
- 85K programmable logic elements
- 64 MB SDRAM


## Hard processor system (HPS)

- Dual-core ARM
- 2 hard memory controllers
- Runs Linux and “bare metal” apps
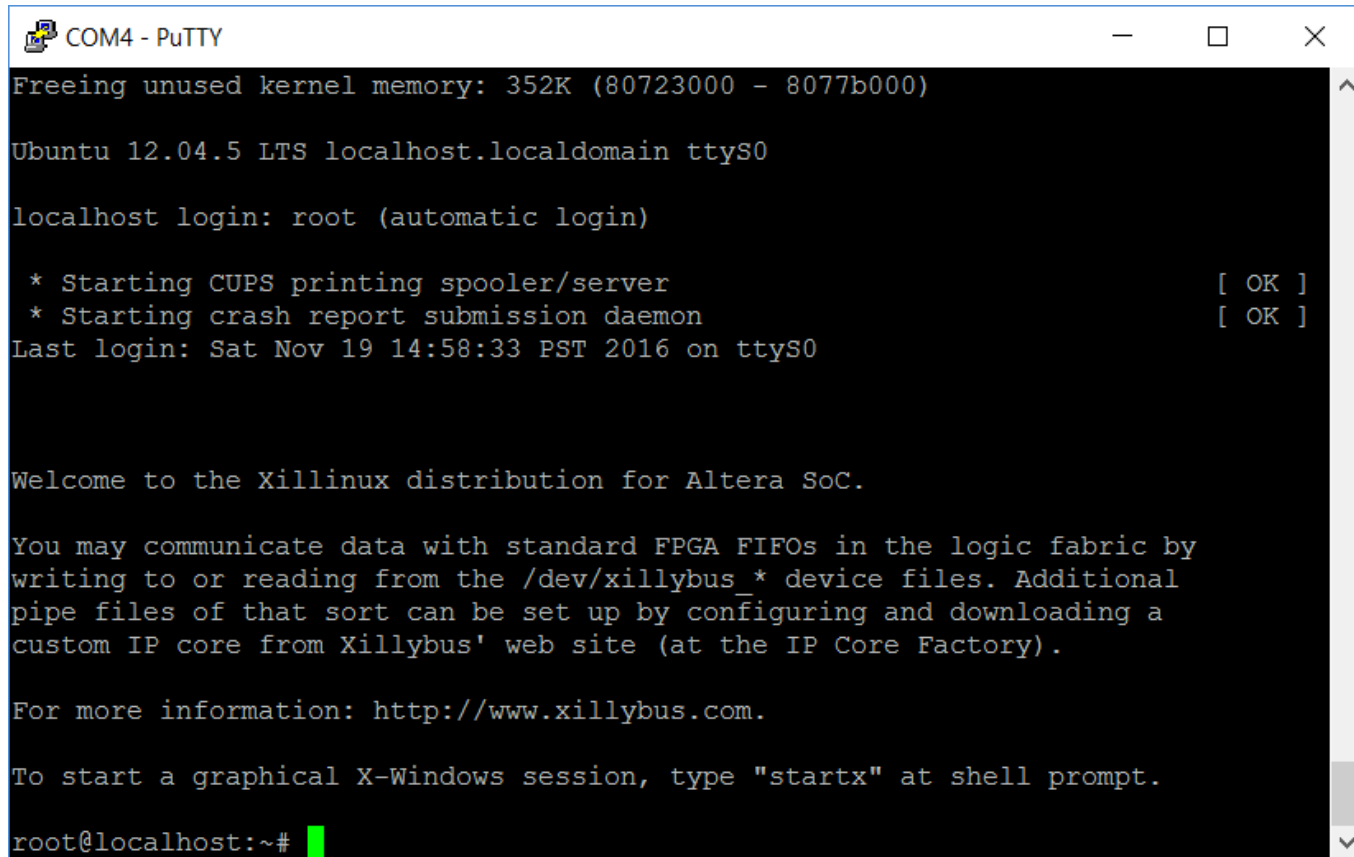
## Board

- 6 seven segment displays
- 10 switches
- 10 LEDs
- 4 pushbuttons
- 2 40-pin GPIO headers
- 1 GB DDR3 SDRAM
- + Micro SD, USB, Ethernet, VGA, ADC, keyboard, mouse, audio, video

Able to boot Ubuntu Linux from a Micro SD card as a command window via PuTTY.



```
COM4 - PuTTY
Freeing unused kernel memory: 352K (80723000 - 8077b000)
Ubuntu 12.04.5 LTS localhost.localdomain ttyS0
localhost login: root (automatic login)
* Starting CUPS printing spooler/server [ OK ]
* Starting crash report submission daemon [ OK ]
Last login: Sat Nov 19 14:58:33 PST 2016 on ttyS0

Welcome to the Xilinx distribution for Altera SoC.

You may communicate data with standard FPGA FIFOs in the logic fabric by
writing to or reading from the /dev/xillybus_* device files. Additional
pipe files of that sort can be set up by configuring and downloading a
custom IP core from Xillybus' web site (at the IP Core Factory).

For more information: http://www.xillybus.com.

To start a graphical X-Window session, type "startx" at shell prompt.

root@localhost:~#
```

With a keyboard, mouse and VGA display, it runs the Ubuntu desktop.

# Software environment

## **Quartus Prime**

The Intel/Altera IDE for compiling Verilog to the FPGA, including SystemBuilder to create a new DE1-SoC project.



## **SignalTap II**

A remote logic analyzer that can be compiled onto the FPGA along with your own code.

## **ModelSim**

The Verilog simulator.

# Digital vs. Analog

 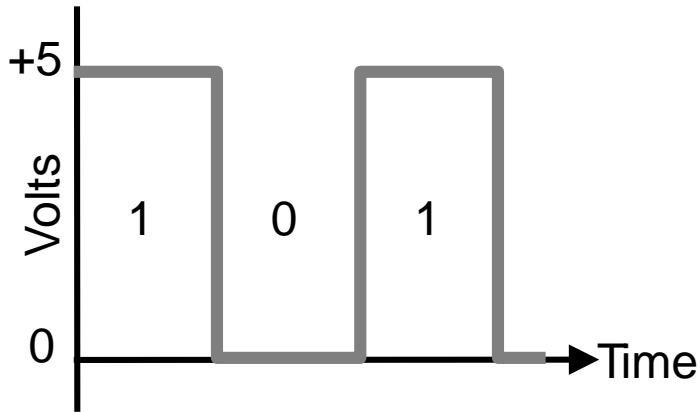

**Digital** means data is represented by *discrete* values.

**Binary/Boolean** means we use only 2 values.

1 = Yes, on, 5 V, high, TRUE  
0 = No, off, 0 V, low, FALSE

**Analog** means the values vary *continuously* over a possibly very broad range.

# Digital representation of information

Typical kinds of data we might like to represent in a digital form:

Numbers

Characters

Music

Video



# Advantages of Digital Circuits

1. Analog systems: slight error in input yields large error in output
2. Digital systems more accurate and reliable  
Readily available as self-contained, easy to cascade building blocks
3. Computers use digital circuits internally
4. Interface circuits (i.e., sensors & actuators) often analog


***This course is about logic design, not system design (processor architecture), not circuit design (transistor level)***

# The ASCII character set for representing text

Hex	Dec	Char	Hex	Dec	Char	Hex	Dec	Char	Hex	Dec	Char
0x00	0	<b>NULL</b> null	0x20	32	<b>Space</b>	0x40	64	<b>@</b>	0x60	96	<b>`</b>
0x01	1	<b>SOH</b> Start of heading	0x21	33	<b>!</b>	0x41	65	<b>A</b>	0x61	97	<b>a</b>
0x02	2	<b>STX</b> Start of text	0x22	34	<b>"</b>	0x42	66	<b>B</b>	0x62	98	<b>b</b>
0x03	3	<b>ETX</b> End of text	0x23	35	<b>#</b>	0x43	67	<b>C</b>	0x63	99	<b>c</b>
0x04	4	<b>EOT</b> End of transmission	0x24	36	<b>\$</b>	0x44	68	<b>D</b>	0x64	100	<b>d</b>
0x05	5	<b>ENQ</b> Enquiry	0x25	37	<b>%</b>	0x45	69	<b>E</b>	0x65	101	<b>e</b>
0x06	6	<b>ACK</b> Acknowledge	0x26	38	<b>&amp;</b>	0x46	70	<b>F</b>	0x66	102	<b>f</b>
0x07	7	<b>BELL</b> Bell	0x27	39	<b>'</b>	0x47	71	<b>G</b>	0x67	103	<b>g</b>
0x08	8	<b>BS</b> Backspace	0x28	40	<b>(</b>	0x48	72	<b>H</b>	0x68	104	<b>h</b>
0x09	9	<b>TAB</b> Horizontal tab	0x29	41	<b>)</b>	0x49	73	<b>I</b>	0x69	105	<b>i</b>
0x0A	10	<b>LF</b> New line	0x2A	42	<b>*</b>	0x4A	74	<b>J</b>	0x6A	106	<b>j</b>
0x0B	11	<b>VT</b> Vertical tab	0x2B	43	<b>+</b>	0x4B	75	<b>K</b>	0x6B	107	<b>k</b>
0x0C	12	<b>FF</b> Form Feed	0x2C	44	<b>,</b>	0x4C	76	<b>L</b>	0x6C	108	<b>l</b>
0x0D	13	<b>CR</b> Carriage return	0x2D	45	<b>-</b>	0x4D	77	<b>M</b>	0x6D	109	<b>m</b>
0x0E	14	<b>SO</b> Shift out	0x2E	46	<b>.</b>	0x4E	78	<b>N</b>	0x6E	110	<b>n</b>
0x0F	15	<b>SI</b> Shift in	0x2F	47	<b>/</b>	0x4F	79	<b>O</b>	0x6F	111	<b>o</b>
0x10	16	<b>DLE</b> Data link escape	0x30	48	<b>0</b>	0x50	80	<b>P</b>	0x70	112	<b>p</b>
0x11	17	<b>DC1</b> Device control 1	0x31	49	<b>1</b>	0x51	81	<b>Q</b>	0x71	113	<b>q</b>
0x12	18	<b>DC2</b> Device control 2	0x32	50	<b>2</b>	0x52	82	<b>R</b>	0x72	114	<b>r</b>
0x13	19	<b>DC3</b> Device control 3	0x33	51	<b>3</b>	0x53	83	<b>S</b>	0x73	115	<b>s</b>
0x14	20	<b>DC4</b> Device control 4	0x34	52	<b>4</b>	0x54	84	<b>T</b>	0x74	116	<b>t</b>
0x15	21	<b>NAK</b> Negative ack	0x35	53	<b>5</b>	0x55	85	<b>U</b>	0x75	117	<b>u</b>
0x16	22	<b>SYN</b> Synchronous idle	0x36	54	<b>6</b>	0x56	86	<b>V</b>	0x76	118	<b>v</b>
0x17	23	<b>ETB</b> End transmission block	0x37	55	<b>7</b>	0x57	87	<b>W</b>	0x77	119	<b>w</b>
0x18	24	<b>CAN</b> Cancel	0x38	56	<b>8</b>	0x58	88	<b>X</b>	0x78	120	<b>x</b>
0x19	25	<b>EM</b> End of medium	0x39	57	<b>9</b>	0x59	89	<b>Y</b>	0x79	121	<b>y</b>
0x1A	26	<b>SUB</b> Substitute	0x3A	58	<b>:</b>	0x5A	90	<b>Z</b>	0x7A	122	<b>z</b>
0x1B	27	<b>FSC</b> Escape	0x3B	59	<b>;</b>	0x5B	91	<b>[</b>	0x7B	123	<b>{</b>
0x1C	28	<b>FS</b> File separator	0x3C	60	<b>&lt;</b>	0x5C	92	<b>\</b>	0x7C	124	<b> </b>
0x1D	29	<b>GS</b> Group separator	0x3D	61	<b>=</b>	0x5D	93	<b>]</b>	0x7D	125	<b>}</b>
0x1E	30	<b>RS</b> Record separator	0x3E	62	<b>&gt;</b>	0x5E	94	<b>^</b>	0x7E	126	<b>~</b>
0x1F	31	<b>US</b> Unit separator	0x3F	63	<b>?</b>	0x5F	95	<b>_</b>	0x7F	127	<b>DEL</b>

Image source: <https://www.pinterest.com/pin/569494315354562943/>

 (Now being supplanted by UNICODE and UTF-8 to support international character sets.)



Numerous audio, image and video file formats.

Specialized hardware to encode or decode the data.


Analog-to-digital (A/D) and digital-to-analog (D/A) converters

Figure 1.7. Using digital technology to represent music.
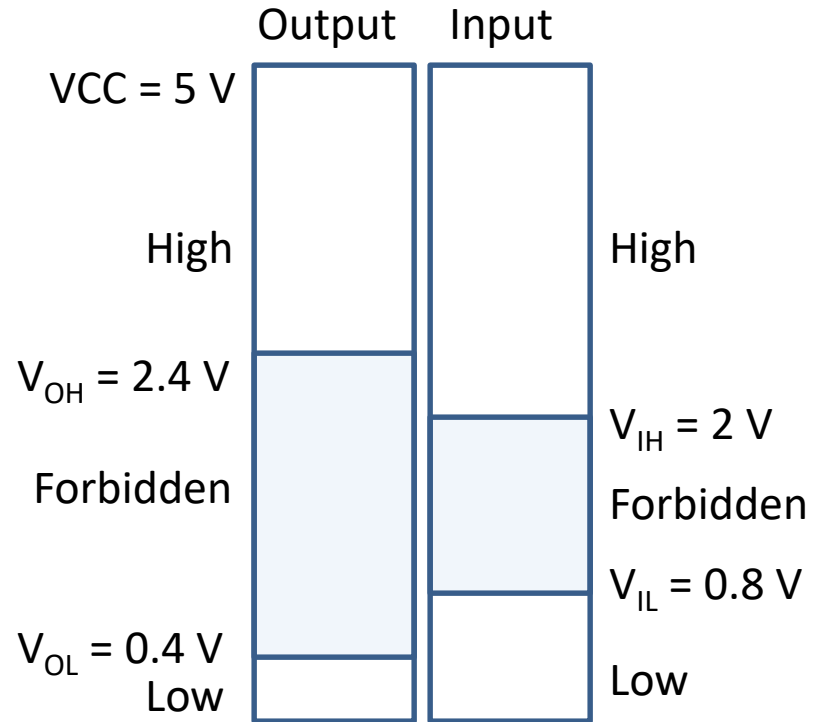
# We only have bits

We represent everything in bits, where each bit can be only a 0 or a 1.

Implemented as voltage levels in a digital circuit, e.g., shown here for TTL.



# Binary numbers

The one data format we care about in this class.

# Binary numbers

Strings of bits.


Like decimal numbers  
but with only 1's and 0's.

**1011**

# Numbers are positional


In decimal

1492

 

In binary


1011

 

# Numbers are positional


In decimal

1492

 

In binary

1011

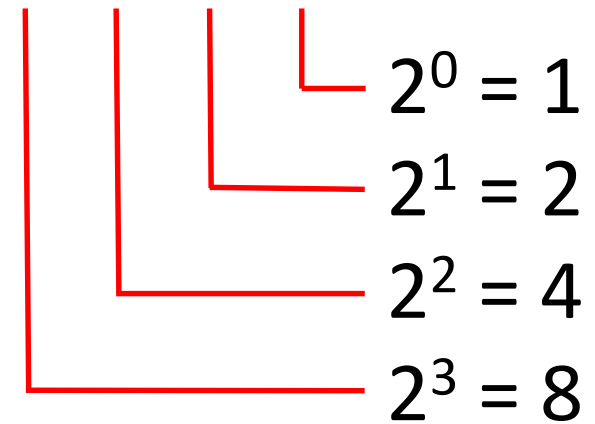



Adding zeroes to the left doesn't change the value.

In decimal

$$001492 = 1492$$

In binary

$$001011 = 1011$$

When we add numbers we get carries.

In decimal

*110*

1492

+ 525

---

2017

In binary

*011*

1011

+ 011

---

1110

# Hex

1. Hard to read long strings of nothing but 1's and 0's.
2. So we break it up into groups of 4 bits called *nibbles*, starting *at the LSB*.
3. Take each 4-bit group as a value from 0 to 15.
4. Values 10 to 15 written as A to F.

0111010010011111


0111 0100 1001 1111

7 4 9 F


Binary	Decimal	Hex
0000	0	0
0001	1	1
0010	2	2
0011	3	3
0100	4	4
0101	5	5
0110	6	6
0111	7	7
1000	8	8
1001	9	9
1010	10	A
1011	11	B
1100	12	C
1101	13	D
1110	14	E
1111	15	F

In hex

A12D

 

# A12D

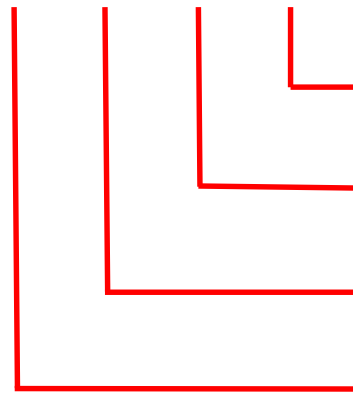


13	*	16 <sup>0</sup>	=	13
2	*	16 <sup>1</sup>	=	32
1	*	16 <sup>2</sup>	=	256
10	*	16 <sup>3</sup>	=	40960

---

41261

# Binary numbers

 


Numbering of the individual bits is from least significant bit (LSB) to most significant bit (MSB).

If  $b_0 = 0$ , the number is even.

If  $b_0 = 1$ , the number is odd.

Each bit represents a power of 2.

# Value of a binary number

 

$$Value = \sum_{i=0}^{n-1} b_i 2^i$$

# Hex

1. Hard to read long strings of nothing but 1's and 0's.

0111010010011111

2. So we break it up into groups of 4 bits at a time, starting *at the LSB*.

0111 0100 1001 1111

3. Take each 4-bit group as a value from 0 to 15.

7 4 9 F

4. Values 10 to 15 written as A to F.



# Hexadecimal base 16 notation

Binary	Decimal	Hex
0000	0	0
0001	1	1
0010	2	2
0011	3	3
0100	4	4
0101	5	5
0110	6	6
0111	7	7
1000	8	8
1001	9	9
1010	10	A
1011	11	B
1100	12	C
1101	13	D
1110	14	E
1111	15	F

# Exercise

What is binary 10100101 in decimal and hex?

# Exercise

What is binary 10100101 in decimal and hex?

$$\begin{aligned}\text{Value} &= 1*1 + 0*2 + 1*4 + 0*8 + 0*16 \\ &\quad + 1*32 + 0*64 + 1*128 \\ &= 1 + 4 + 32 + 128 \\ &= 165\end{aligned}$$

$$\begin{aligned}10100101 &= 1010\ 0101 = \text{A5 hex} \\ &= \text{A5} = 10*16 + 5 = 165\end{aligned}$$

# Exercise

What is binary 1111100 in decimal and hex?

# Exercise

What is binary 1111100 in decimal and hex?

$$\begin{aligned}\text{Value} &= 0*1 + 0*2 + 1*4 + 1*8 + 1*16 + 1*32 + 1*64 \\ &= 4 + 8 + 16 + 32 + 64 \\ &= 124\end{aligned}$$

Only 7 bits given, extend with high-order zeros.

$$\begin{aligned}10100101 &= 111\ 1100 = 0111\ 1100 = 7C\ \text{hex} \\ &= 7*16 + 12 = 124\end{aligned}$$

# Converting to binary

1. Repeatedly integer divide by 2 until the result is 0.
2. At each step, the remainder is the next bit, starting with the LSB.

Convert 12 to binary

Value	Result	Remainder	
12	6	0	LSB
6	3	0	
3	1	1	
1	0	1	MSB

(We start at the LSB because the lowest bit is just odd or even.)

12 base 10 = 1100 binary = Hex C

Exercise: Convert 957 to binary

Value	Result	Remainder
957		

## Exercise: Convert 957 to binary

Value	Result	Remainder	
957	478	1	LSB
478	239	0	
239	119	1	
119	59	1	
59	29	1	
29	14	1	
14	7	0	
7	3	1	
3	1	1	
1	0	1	MSB

957 decimal = 11 1011 1101 binary = 3BD hex



## Exercise: Convert 1492 to hex

Value	Result	Remainder
1492		

## Exercise: Convert 1492 to hex

Value	Result	Remainder	
1492	746	0	LSB
746	373	0	
373	186	1	
186	93	0	
93	46	1	
46	23	0	
23	11	1	
11	5	1	
5	2	1	
2	1	0	
1	0	1	MSB

1492 decimal = 101 1101 0100 binary = 5D4 hex

# Chapter 2

## Introduction to Logic Circuits

# Example: Warning lights in a car

1. DoorAjar ( DriverDoorOpen, PassengerDoorOpen )
2. HighBeamIndicator ( LightsOn, HighBeams )

# Example: Warning lights in a car

1. DoorAjar ( DriverDoorOpen, PassDoorOpen )

DoorAjar = DriverDoorOpen OR PassengerDoorOpen

2. HighBeamIndicator ( LightsOn, HighBeams ):

HighBeamIndicator = LightsOn AND HighBeams

# Example: Warning lights in a car

3. SeatBeltLight ( DriverBeltIn )
4. SeatBeltLight ( DriverBeltIn, PassengerBeltIn, PassengerPresent )

# Example: Warning lights in a car

3. SeatBeltLight ( DriverBeltIn )

SeatBeltLight = NOT DriverBeltIn


4. SeatBeltLight ( DriverBeltIn, PassengerBeltIn,  
PassengerPresent )

SeatBeltLight = NOT DriverBeltIn OR  
PassengerPresent AND NOT PassengerBeltIn

(We prioritize NOT before AND before OR.)
 
# Boolean algebra

Named after George Boole, who published an algebraic description of the processes involved in logical thought and reasoning in 1849.



[https://en.wikipedia.org/wiki/George\\_Boole](https://en.wikipedia.org/wiki/George_Boole)



# Boolean algebra

In the 1930s, used by Claude Shannon to describe circuits built with switches, and thus with logic circuits.



[https://en.wikipedia.org/wiki/Claude\\_Shannon](https://en.wikipedia.org/wiki/Claude_Shannon)

# ax·i·om

/'aksēəm/

*noun*

a statement or proposition that is regarded as being established, accepted, or self-evidently true.

"the **axiom** that supply equals demand"

synonyms: accepted truth, general truth, [dictum](#), [truism](#), [principle](#); [More](#)

- MATHEMATICS

a statement or proposition on which an abstractly defined structure is based.

# Axioms of Boolean Algebra

1a.  $0 \bullet 0 = 0$

1b.  $1 + 1 = 1$

2a.  $1 \bullet 1 = 1$

2b.  $0 + 0 = 0$



3a.  $0 \bullet 1 = 1 \bullet 0 = 0$

3b.  $1 + 0 = 0 + 1 = 1$

4a. If  $x = 0$ , then  $x' = 1$



4b. If  $x = 1$ , then  $x' = 0$

Notice the *duality*:

  
  
# Duality

Given any logic expression, its dual is obtained by swapping all the + and • operators and ones and zeros.



# Single-variable theorems

$$5a. \quad x \bullet 0 = 0$$

$$5b. \quad x + 1 = 1$$

$$6a. \quad x \bullet 1 = x$$

$$6b. \quad x + 0 = x$$

$$7a. \quad x \bullet x = x \quad \text{Replication}$$

$$7b. \quad x + x = x$$

$$8a. \quad x \bullet x' = 0$$

$$8b. \quad x + x' = 1$$

$$9. \quad (x')' = x$$

Easily proved by *perfect induction*, trying all the possibilities.


# Boolean Algebra

Values	0, 1
Variables	A, B, C, Sum, DoorOpen, ..
Operations	<b>NOT, AND, OR, XOR</b>


<i>Operation</i>	<i>Written as</i>
<b>NOT</b> a	$\bar{a}$ or $a'$
a <b>AND</b> b	$a \bullet b$ or $a b$
a <b>OR</b> b	$a + b$
a <b>XOR</b> b	$a \wedge b$
 
# The basic gates.


**AND** If all inputs are true, the output is true.










 
**OR** If any input is true, the output is true.



 **NOT** The output is the inverse of the input.



## A more complete set of gates

        



# Truth tables

We describe Boolean functions with truth tables.

a	b	a <b>AND</b> b
0	0	0
0	1	0
1	0	0
1	1	1


a	b	a <b>OR</b> b
0	0	0
0	1	1
1	0	1
1	1	1

a	b	a <b>XOR</b> b
0	0	0
0	1	1
1	0	1
1	1	0

a	<b>NOT</b> a
0	1
1	0

a	0	0	1	1
+b	+0	+1	+0	+1
s1 s0	0 0	0 1	0 1	1 0

a	b	s1	s0
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 

Addition of one-bit binary numbers.

# Truth tables

Deriving Boolean equations from truth tables:

a	b	s1	s0
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

OR together *product* terms for each truth table row where the function is 1.

If input variable is 0, it appears in complemented form; if 1, it appears uncomplemented.

# Truth tables

Deriving Boolean equations from truth tables:

a	b	s1	s0
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$s0 = a \wedge b$$

$$s1 = a \oplus b$$

# Example: a full adder

A	B	Cin	Cout	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Sum =

Cout =

# Example: a full adder

A	B	Cin	Cout	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$\text{Sum} = A' B' \text{Cin} + A' B \text{Cin}' + A B' \text{Cin}' + A B \text{Cin}$$

$$\text{Cout} = A' B \text{Cin} + A B' \text{Cin} + A B \text{Cin}' + A B \text{Cin}$$