

BEE 271 Digital circuits and systems

Spring 2017

Lecture 7: Multiplexers and Shannon's expansion

Nicole Hamilton


<https://faculty.washington.edu/kd1uj>

Topics

1. Signed numbers
2. Adders
3. Multiplexers
4. Shannon's expansion

MSB


LSB

 

Unsigned binary

Sign MSB

LSB

 

Signed binary

$b_3 b_2 b_1 b_0$	Sign and magnitude	1's complement	2's complement
0111	+7	+7	+7
0110	+6	+6	+6
0101	+5	+5	+5
0100	+4	+4	+4
0011	+3	+3	+3
0010	+2	+2	+2
0001	+1	+1	+1
0000	+0	+0	+0
1000	-0	-7	-8
1001	-1	-6	-7
1010	-2	-5	-6
1011	-3	-4	-5
1100	-4	-3	-4
1101	-5	-2	-3
1110	-6	-1	-2
1111	-7	-0	-1

Table 3.2. Interpretation of four-bit signed integers.

Sign + magnitude

$b_3 b_2 b_1 b_0$	Sign and magnitude
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-0
1001	-1
1010	-2
1011	-3
1100	-4
1101	-5
1110	-6
1111	-7

The first bit is the sign (+ or -) and the rest of the bits are the value as a positive binary number.

For example, in 4-bit sign + magnitude:

$$+5 = 0101$$

$$-5 = 1101$$

Problem with sign + magnitude

$b_3 b_2 b_1 b_0$	Sign and magnitude
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-0
1001	-1
1010	-2
1011	-3
1100	-4
1101	-5
1110	-6
1111	-7

But if the signs are different, it doesn't work.

$$\begin{array}{r} 1010 \quad (-2) \\ + 0011 \quad (+3) \\ \hline 1101 \quad (-5) \end{array}$$

Wrong

Must compare and subtract the smaller from the larger and use the sign of the larger for the result.

$$\begin{array}{r} 011 \quad (+3) \\ - 010 \quad (-2 \text{ w/o the sign}) \\ \hline 001 \end{array}$$

1's complement

$b_3 b_2 b_1 b_0$	1's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-7
1001	-6
1010	-5
1011	-4
1100	-3
1101	-2
1110	-1
1111	-0

The first bit is the sign (+ or -) and the rest of the bits are the value as a binary number if it's positive or with the bits inverted if it's negative.

For example, in 4-bit 1's complement:

$$+5 = 0101$$

$$-5 = 1010$$

Notice that 0 has two values: 0000 (+0) and 1111 (-0).

Adding in 1's complement

$b_3 b_2 b_1 b_0$	1's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-7
1001	-6
1010	-5
1011	-4
1100	-3
1101	-2
1110	-1
1111	-0

If both operands are positive,
adding works, not other wise.

$$\begin{array}{r} 0010 \\ + 0011 \\ \hline 0101 \end{array}$$

$$\begin{array}{r} 1101 \\ + 1100 \\ \hline 1001 \end{array}$$

(-6) Wrong

2's complement

$b_3 b_2 b_1 b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

The first bit is the sign (+ or -) and the rest of the bits are the value as a binary number if it's positive or 2^n minus the value if it's negative.

For example, in 4-bit 2's complement:

$$+5 = 0101$$

$$-5 = 1011$$

Notice that adding these as unsigned numbers $0101 + 1011 = 10000 = 2^n$, which overflows to 0.

2's complement

$b_3 b_2 b_1 b_0$	2's complement
0111	+7
0110	+6
0101	+5
0100	+4
0011	+3
0010	+2
0001	+1
0000	+0
1000	-8
1001	-7
1010	-6
1011	-5
1100	-4
1101	-3
1110	-2
1111	-1

Let K be the negative equivalent of an n-bit positive number P.

Then, in 2's complement representation K is obtained by subtracting P from 2^n , namely

$$K = 2^n - P$$

Deriving 2's complement

For a positive n-bit number P , let K_1 and K_2 denote its 1's and 2's complements, respectively.

$$K_1 = (2^n - 1) - P$$
$$K_2 = 2^n - P$$

Since $K_2 = K_1 + 1$, the 2's complement can be computed by inverting all bits of P and then adding 1.

```
module TwosComplementA( input [ 15:0 ] A,
    output [ 15:0 ] minusA );

    assign minusA = ~A + 1;

endmodule
```

Two's complement in Verilog.

```
module TwosComplementB( input [ 15:0 ] A,
    output [ 15:0 ] minusA );

    assign minusA = -A;

endmodule
```

Two's complement in Verilog.

```
module TwosComplementC( input signed [ 15:0 ] A,  
    output signed [ 15:0 ] minusA );  
  
    assign minusA = -A;  
  
endmodule
```

Two's complement in Verilog.

Subtraction in Two's Complement

$$A - B = A + (-B) = A + \sim B + 1$$

1) 0010 - 0110

2) 1011 - 1001

3) 1011 - 0001

Subtraction in Two's Complement

$$A - B = A + (-B) = A + \sim B + 1$$

1) $0010 - 0110$

$+2 \quad +6$

0010 (+2)
1001 (~6)
0001 (+1)
1100 (-4)

2) $1011 - 1001$

3) $1011 - 0001$

Subtraction in Two's Complement

$$A - B = A + (-B) = A + \sim B + 1$$

1) 0010 - 0110

1011 (-5)

0110 (~-7)

0001 (+1)

0010 (+2)

2) 1011 - 1001

-5 -7

3) 1011 - 0001

Subtraction in Two's Complement

$$A - B = A + (-B) = A + \sim B + 1$$

1) 0010 - 0110

2) 1011 - 1001

3) 1011 - 0001

-5 +1

1011 (-5)

1110 (~1)

0001 (+1)

1010 (-6)

Sign Extension

To convert from N-bit to M-bit 2's Complement ($N < M$),
simply duplicate sign bit:

1. Convert $(0010)_2$ to 8-bit 2's Complement

2. Convert $(1011)_2$ to 8-bit 2's Complement

Sign Extension

To convert from N-bit to M-bit 2's Complement (N<M),
simply duplicate sign bit:

1. Convert $(0010)_2$ to 8-bit 2's Complement

0000 0010

2. Convert $(1011)_2$ to 8-bit 2's Complement

1111 1011

```
module SignExtendA( input [ 7:0 ] a,
                     output [ 15:0 ] b );
    // Sign-extend both a, replicating A[ 7 ]
    // through eight positions.

    assign b = { { 8 { a[ 7 ] } }, a };

endmodule
```

Sign extend in Verilog using replication and concatenation.

```
module SignExtendB( input signed [ 7:0 ] a,
                     output signed [ 15:0 ] b );
    // Let the compiler sign-extend a using
    // the signed keyword.

    assign b = a;

endmodule
```

Sign extend in Verilog using the signed keyword.

```
module AddUnsigned( input [ 3:0 ] A, input [ 7:0 ] B,
    output [ 9:0 ] sum );
    // Verilog pads high-order bits with zeros.

    assign sum = A + B;

endmodule
```

Adding unsigned numbers of different sizes in Verilog.

```
module AddSignedA( input [ 3:0 ] A, input [ 7:0 ] B,
    output [ 9:0 ] sum );

    // Must sign-extend both A and B, replicating
    // A[ 3 ] through six positions and B[ 7 ] through
    // two positions.

    assign sum = { { 6{ A[ 3 ] } }, A } +
                { 2{ B[ 7 ] } }, B };

endmodule
```

Adding signed numbers of different sizes in Verilog.

```
module AddSignedB( input signed [ 3:0 ] A,
                   input signed [ 7:0 ] B,
                   output signed [ 9:0 ] sum );


  // Let the compiler sign-extend A and B using
  // the signed keyword.

  assign sum = A + B;


endmodule
```

Adding signed numbers of different sizes in Verilog.

Unsigned addition

 

Signed addition

 

Processor instruction sets have both carry and overflow status bits so only one add instruction is needed for either signed or unsigned addition.

```
module AdderWithOverflowA( input [ 15:0 ] a, b,
    output [ 15:0 ] s, carryOut, overflow );

    // Carryout is a carry from the MSB in
    // unsigned arithmetic.

    // Overflow is a carry from the MSB in
    // signed arithmetic into the sign bit.

    assign { carryOut, s } = a + b,
        overflow = a[ 15 ] == b[ 15 ] &&
                    a[ 15 ] != s[ 15 ];

endmodule
```

Overflow and carry detection in Verilog.

```
module AdderWithOverflowB( input [ 15:0 ] a, b,
    output [ 15:0 ] s, carryOut, overflow );

    // Carryout is a carry from the MSB in
    // unsigned arithmetic.

    // Overflow is a carry from the MSB in
    // signed arithmetic into the sign bit.

    assign { carryOut, s } = a + b,
        overflow = ~a[ 15 ] & ~b[ 15 ] & s[ 15 ] |
                    a[ 15 ] & b[ 15 ] & ~s[ 15 ];

endmodule
```

Overflow and carry detection in Verilog.

```

module AdderWithOverflowC( input [ 15:0 ] a, b,
    output [ 15:0 ] s, carryOut, output reg overflow );

    // Carryout is a carry from the MSB in
    // unsigned arithmetic.

    // Overflow is a carry from the MSB in
    // signed arithmetic into the sign bit.

    wire [ 0:2 ] signbits= { a[ 15 ], b[ 15 ], s[ 15 ] };
    assign { carryOut, s } = a + b;

    always @(*)
        case ( signbits )
            'b001, 'b110: overflow = 1;
            default: overflow = 0;
        endcase

endmodule

```

Overflow and carry detection in Verilog.

```
module AdderWithOverflowD( input [ 15:0 ] a, b,
                           output [ 15:0 ] s, carryOut, overflow );

  // Carryout is a carry from the MSB in
  // unsigned arithmetic.

  // Overflow is a carry from the MSB in
  // signed arithmetic into the sign bit.

  wire [ 0:2 ] signbits = { a[ 15 ], b[ 15 ], s[ 15 ] };
  assign { carryOut, s } = a + b,
         overflow = signbits == 'b001 || signbits == 'b110;

endmodule
```

Overflow and carry detection in Verilog.

Adders

When we add numbers we get carries.


In decimal

$$\begin{array}{r} 110 \\ 1492 \\ + 525 \\ \hline 2017 \end{array}$$


In binary

$$\begin{array}{r} 011 \\ 1011 \\ + 011 \\ \hline 1110 \end{array}$$

$$\begin{array}{r}
 a \\
 + b \\
 \hline
 c \ s
 \end{array}
 \quad
 \begin{array}{c|c}
 0 & 0 \\
 0 & +1 \\
 \hline
 0 & 1 \\
 1 & +0 \\
 \hline
 1 & 0
 \end{array}
 \quad
 \begin{array}{c|c}
 1 & 1 \\
 +0 & \\
 \hline
 0 & 1
 \end{array}
 \quad
 \begin{array}{c|c}
 1 & 1 \\
 +1 & \\
 \hline
 1 & 0
 \end{array}$$

 

a	b	c	s
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 

Addition of one-bit binary numbers.

c_i	x_i	y_i	c_{i+1}	s_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

(a) Truth table

c_i	$x_i y_i$	00	01	11	10
0			1		
1		1		1	

$$s_i = x_i \oplus y_i \oplus c_i$$

c_i	$x_i y_i$	00	01	11	10
0				1	
1			1	1	1

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

(b) Karnaugh maps



 


Figure 3.3. Full-adder.

 


Block diagram

 

Detailed diagram

A full adder built using half adders.

 

An n -bit ripple-carry adder.


```

module FullAdderA( input cin, a, b,
                    output s, cout );

    wire x, y, z;
    xor ( s, a, b, cin );
    and ( x, a, b );
    and ( y, a, cin );
    and ( z, b, cin );
    or ( cout, x, y, z );

endmodule

```

 

A full adder in Verilog.


```

module FullAdderB( input cin, a, b,
                    output s, cout );

    wire x, y, z;
    xor ( s, a, b, cin );
    and ( x, a, b ),
          ( y, a, cin ),
          ( z, b, cin );
    or ( cout, x, y, z );

endmodule

```

 


A full adder in Verilog.

```

module FullAdderC( input cin, a, b,
                    output s, cout );
    assign s = a ^ b ^ cin;
    assign cout = a & b | a & cin | b & cin;
endmodule

```

 


A full adder in Verilog.

```


module FullAdderD( input cin, a, b,
                    output s, cout );
  assign s = a ^ b ^ cin,
        cout = a & b | a & cin | b & cin;
endmodule

```

 

A full adder in Verilog.
 
```
module FullAdderE( input cin, a, b,  
    output s, cout );  
  
    assign { cout, s } = a + b + cin;  
  
endmodule
```



A full adder in Verilog.


```

module FourBitAdderA( input cin, input [ 3:0 ] a, b,
                      output cout, output [ 3:0 ] s );

  wire [ 3:1 ] c;
  FullAdderE( cin,      a[ 0 ], b[ 0 ], s[ 0 ], c[ 1 ] );
  FullAdderE( c[ 1 ],    a[ 1 ], b[ 1 ], s[ 1 ], c[ 2 ] );
  FullAdderE( c[ 2 ],    a[ 2 ], b[ 2 ], s[ 2 ], c[ 3 ] );
  FullAdderE( c[ 3 ],    a[ 3 ], b[ 3 ], s[ 3 ], cout );

endmodule

```

 

A 4-bit adder in Verilog.

```
module NBitAdderA( input cin, input [ n - 1:0 ] a, b,
    output cout, output [ n - 1:0 ] s );

parameter n = 16;
wire [ n:0 ] c;
assign c[ 0 ] = cin,
      cout    = c[ n ];

generate
    genvar i;
    for ( i = 0; i <= n; i = i + 1 )
        begin : fa
            FullAdderE stage( c[ i ], a[ i ], b[ i ], s[ i ],
                c[ i + 1 ] );
        end
endgenerate

endmodule
```

An n-bit adder in Verilog.

```
module NBitAdderB( input cin, input [ n - 1:0 ] a, b,
    output reg cout, output reg [ n - 1:0 ] s );

parameter n = 16;
reg [ n:0 ] c;
integer i;

always @(*)
begin
c[ 0 ] = cin;
for ( i = 0; i < n; i = i + 1 )
begin
    s[ i ] = a[ i ] ^ b[ i ] ^ c[ i ];
    c[ i + 1 ] = a[ i ] & b[ i ] |
                    a[ i ] & c[ i ] |
                    b[ i ] & c[ i ];
end
cout = c[ n ];
end

endmodule
```

An n-bit adder in Verilog.

```
module NBitAdderC( input cin, input [ n - 1:0 ] a, b,
    output reg cout, output reg [ n - 1:0 ] s );

parameter n = 16;

always @(*)
begin
    reg [ n:0 ] c;
    integer i;
    c[ 0 ] = cin;
    for ( i = 0; i < n; i = i + 1 )
        begin
            s[ i ] = a[ i ] ^ b[ i ] ^ c[ i ];
            c[ i + 1 ] = a[ i ] & b[ i ] |
                            a[ i ] & c[ i ] |
                            b[ i ] & c[ i ];
        end
    cout = c[ n ];
end

endmodule
```

An n-bit adder in Verilog.

```
module NBitAdderD( input cin, input [ n - 1:0 ] a, b,
    output cout, output [ n - 1:0 ] s );

parameter n = 16;
assign { cout, s } = a + b + cin;

endmodule
```

An n-bit adder in Verilog.

 
 



Figure 3.6. Circuit that multiplies an eight-bit unsigned number by 3.

{ cn, s } = Subtract ? x - y : x + y

$$-y = \sim y + 1$$

$$y \wedge 1 = \sim y$$

$$y \wedge 0 = y$$

 

An adder/subtractor unit

Critical path

Performance

Measure the largest delay from operands being presented as inputs until all output bits are valid.



Often referred to as the *critical path delay*.

Performance

Performance gains often come from insights into how to structure a problem, e.g., into *layers*, *modules* or *hierarchies*, thus allowing an efficient solution.

These are often called *architectural* decisions.

  Addition offers a classic example where an insight about when carries are generated or propagated allows a dramatic shortening of the critical path.



An n -bit ripple-carry adder has 2 gate delays per bit.

Generate & propagate

$$c_{i+1} = a_i b_i + a_i c_i + b_i c_i$$

$$c_{i+1} = a_i b_i + (a_i + b_i) c_i$$

$$g_i = a_i b_i = \textcolor{red}{Generate\ carry}$$


$$p_i = a_i + b_i = \textcolor{red}{Propagate\ carry}$$

$$c_{i+1} = g_i + p_i c_i$$

Generate & propagate

By themselves, generate and propagate offer no advantage if all you do is build a ripple adder.

It just adds one more gate delay.

 

A ripple adder using carry propagate and carry generate.
Delay = $2n + 1$ gate delays, where n = number of stages (bits)

Carry-lookahead

The key insight that all of the g_i and p_i terms have only one gate delay.

So it's possible to simply expand terms to figure out whether a carry into an *entire block* of, say 4 or 8 or 16 bits, will generate a carry out

You can do that with only two more gate delays if you have gates with enough inputs.

This is called *carry-lookahead*.

 


Figure 3.15. The first two stages of a carry-lookahead adder.

Carry lookahead

$$c_{i+1} = g_i + p_i c_i$$

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1(g_0 + p_0 c_0) = g_1 + p_1 g_0 + p_1 p_0 c_0$$

$$c_3 = g_2 + p_2(g_1 + p_1 g_0 + p_1 p_0 c_0)$$

$$= g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$$

⋮

$$c_{i+1} = g_i + \sum_{j=0}^{i-1} \left(g_j \prod_{k=j+1}^i p_k \right) + c_0 \prod_{k=0}^i p_k$$

 


Figure 3.16. A hierarchical carry-lookahead adder with ripple-carry between blocks.


 
 


Figure 3.17. A hierarchical carry-lookahead adder.

multiplexers and decoders

- A *multiplexer* is a many-to-one function, selecting from a set of inputs (which could be vectors).
- An *encoder* or *decoder* translates from one encoding to another.
 1. Select highest priority.
 2. 4-bit binary to 1-of-16 select.
 3. 4-bit binary to 7-segment display.

The Multiplexer

 


s	f
0	a
1	b

Selects a or b based on s , *multiplexing* these signals onto the output f .

Multiplexer

 1. An element that selects data from one of many input lines and directs it to a single output line
2. Input: 2^N input lines and N selection lines
3. Output: The data from *one* selected input line
4. Multiplexer often abbreviated as MUX




```

module Mux2To1A(
    input s, a, b,
    output f );
    wire g, h, k;
    not ( k, s );
    and ( g, k, a ),
          ( h, s, b );
    or  ( f, g, h );
endmodule


```

Structural code for a multiplexer.

 

```
module Mux2To1D(
    input s, a, b,
    output f );
    assign f = ~s & a | s & b;
endmodule
```

Continuous assignment.

 


```

module Mux2To1F(
    input s, a, b,
    output reg f );
    always @( s, a, b )
        if ( s )
            f = b;
        else
            f = a;
endmodule

```


Behavioral description of a multiplexer.

 

Schematic symbol

s_1	s_0	f
0	0	w_0
0	1	w_1
1	0	w_2
1	1	w_3

Truth table

 

Circuit

A 4-to-1 multiplexer.

 


Figure 4.3. Using 2-to-1 multiplexers to build a 4-to-1 multiplexer.


```

module Mux4to1A( input [ 0:3 ] x, input [ 1:0 ] s,
    output f );

    assign f = s == 0 ? x[ 0 ] :
                s == 1 ? x[ 1 ] :
                s == 2 ? x[ 2 ] : x[ 3 ];

endmodule

```

 


A 4-to-1 multiplexer.

```

module Mux4to1B( input [ 0:3 ] x, input [ 1:0 ] s,
    output f );
    assign f = s[ 1 ] ?
        s[ 0 ] ? x[ 3 ] : x[ 2 ] :
        s[ 0 ] ? x[ 1 ] : x[ 0 ];
endmodule

```

 


A 4-to-1 multiplexer.

```

module Mux4to1C( input [ 0:3 ] x, input [ 1:0 ] s,
    output reg f );

    always @(*)
        if ( s == 0 )
            f = x[ 0 ];
        else
            if ( s == 1 )
                f = x[ 1 ];
            else
                if ( s == 2 )
                    f = x[ 2 ];
                else
                    f = x[ 3 ];
endmodule

```

 


A 4-to-1 multiplexer.

```

module Mux4to1D( input [ 0:3 ] x, input [ 1:0 ] s,
    output reg f );

    always @(*)
        case ( s )
            0: f = x[ 0 ];
            1: f = x[ 1 ];
            2: f = x[ 2 ];
            3: f = x[ 3 ];
        endcase
    endmodule

```

 

A 4-to-1 multiplexer.


```

module Mux4to1E( input [ 0:3 ] x, input [ 1:0 ] s,
    output f );

    wire a, b;
    Mux2to1A ma ( x[ 0 ], x[ 1 ], s[ 0 ], a );
    Mux2to1A mb ( x[ 2 ], x[ 3 ], s[ 0 ], b );
    Mux2to1A mf ( a, b, s[ 1 ], f );


endmodule

```

 


A 4-to-1 multiplexer.

 
```
module Mux4to1F( input [ 0:3 ] x, input [ 1:0 ] s,  
    output f );  
  
    assign f = x[ s ];  
  
endmodule
```




A 4-to-1 multiplexer.

 

An 8-to-1 multiplexer.

 

A 16-to-1 multiplexer.

 

A 16-to-1 multiplexer built from 4-to-1 multiplexers.

```
module Mux16to1A( input [ 0:15 ] w,
                   input [ 3:0 ] s, output f );

  wire [ 0:3 ] m;

  Mux4to1 m1 ( w[ 0:3 ], s[ 1:0 ], m[ 0 ] );
  Mux4to1 m2 ( w[ 4:7 ], s[ 1:0 ], m[ 1 ] );
  Mux4to1 m3 ( w[ 8:11 ], s[ 1:0 ], m[ 2 ] );
  Mux4to1 m4 ( w[ 12:15 ], s[ 1:0 ], m[ 3 ] );
  Mux4to1 m5 ( m[ 0:3 ], s[ 3:2 ], f       );

endmodule
```

A16-to-1 multiplexer.

```
module Mux16to1B( input [ 0:15 ] w,
                   input [ 3:0 ] s, output reg f );

  always @(*)
    case ( s )
      0: f = w[ 0 ];
      1: f = w[ 1 ];
      2: f = w[ 2 ];
      3: f = w[ 3 ];
      4: f = w[ 4 ];
      5: f = w[ 5 ];
      6: f = w[ 6 ];
      7: f = w[ 7 ];
      8: f = w[ 8 ];
      9: f = w[ 9 ];
      10: f = w[ 10 ];
      11: f = w[ 11 ];
      12: f = w[ 12 ];
      13: f = w[ 13 ];
      14: f = w[ 14 ];
      15: f = w[ 15 ];
    endcase

  endmodule
```

```
module Mux16to1C( input [ 0:15 ] w,
                   input [ 3:0 ] s, output reg f );

  always @(*)
    begin
      if ( s == 0 ) f = w[ 0 ];
      if ( s == 1 ) f = w[ 1 ];
      if ( s == 2 ) f = w[ 2 ];
      if ( s == 3 ) f = w[ 3 ];
      if ( s == 4 ) f = w[ 4 ];
      if ( s == 5 ) f = w[ 5 ];
      if ( s == 6 ) f = w[ 6 ];
      if ( s == 7 ) f = w[ 7 ];
      if ( s == 8 ) f = w[ 8 ];
      if ( s == 9 ) f = w[ 9 ];
      if ( s == 10 ) f = w[ 10 ];
      if ( s == 11 ) f = w[ 11 ];
      if ( s == 12 ) f = w[ 12 ];
      if ( s == 13 ) f = w[ 13 ];
      if ( s == 14 ) f = w[ 14 ];
      if ( s == 15 ) f = w[ 15 ];
    end

endmodule
```


```
module Mux16to1D( input [ 0:15 ] w,
                   input [ 3:0 ] s, output reg f );

  always @(*)
    begin
      integer p;
      for ( p = 0; p < 16; p = p + 1 )
        if ( s == p )
          f = w[ p ];
    end


endmodule
```

```
module Mux16to1E( input [ 0:15 ] w,
    input [ 3:0 ] s, output f );
    assign f = w[ s ];
endmodule
```

 Synthesis of logic functions using multiplexers




A 2×2 crossbar switch

 

Implementation using multiplexers


A practical application of multiplexers.

w_1	w_2	f
0	0	0
0	1	1
1	0	1
1	1	0

 

Implementation using a 4-to-1 multiplexer

w_1	w_2	f
0	0	0
0	1	1
1	0	1
1	1	0

 


Modified truth table

Circuit



Synthesis of a logic function using multiplexers.

w_1	w_2	w_3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 

Synthesis of 3-input function using an 8-to-1 multiplexer.

  
$$f(a, b, c, d) = \sum m(5, 7, 8, 9, 10, 11, 12, 13, 14)$$



w_1	w_2	w_3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

w_1	w_2	f
0	0	0
0	1	w_3
1	0	w_3
1	1	1

Modified truth table

 


A 3-input majority function using a 4-to-1 multiplexer.

w_1	w_2	w_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$w_2 \wedge w_3$

$(w_2 \wedge w_3)'$

Truth table

 


Circuit

A 3-input XOR implemented with 2-to-1 multiplexers.

w_1	w_2	w_3	f
0	0	0	0
0	0	1	1 } w_3
0	1	0	1 } w_3'
0	1	1	0 } w_3'
1	0	0	1 } w_3'
1	0	1	0 } w_3'
1	1	0	0 } w_3
1	1	1	1 }

Truth table

 

Circuit

A 3-input XOR function implemented with a 4-to-1 multiplexer.


Shannon's expansion theorem

Any Boolean function $f(w_1, w_2, \dots, w_n)$ can be written in the form:

$$f(w_1, w_2, \dots, w_n) = \\ w_1' f(0, w_2, \dots, w_n) \\ + w_1 f(1, w_2, \dots, w_n)$$

$f(0, w_2, \dots, w_n)$ is a *cofactor* of f with respect to w_1' , written $f_{w_1'}$

 $f(1, w_2, \dots, w_n)$ is a *cofactor* of f with respect to w_1 , written f_{w_1}




(a) Shannon's expansion of the function f .

Figure 4.10. The three-input majority function implemented using a 2-to-1 multiplexer.

w_1	w_2	w_3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Truth table

 

Circuit


$$f = w_1' w_3' + w_1 w_2 + w_1 w_3$$

Shannon's expansion for a 2-in mux:


$$\begin{aligned} f &= w_1' f_{w_1'} + w_1 f_{w_1} \\ &= w_1' (w_3') + w_1 (w_2 + w_3) \end{aligned}$$

For a 4-in mux, expand again:
 
$$\begin{aligned} f &= w_1' w_2' f_{w_1' w_2'} + w_1' w_2 f_{w_1' w_2} \\ &\quad + w_1 w_2' f_{w_1 w_2'} + w_1 w_2 f_{w_1 w_2} \\ &= w_1' w_2' (w_3') + w_1' w_2 (w_3') \\ &\quad + w_1 w_2' (w_3) + w_1 w_2 (1) \end{aligned}$$



(a) Using a 2-to-1 multiplexer

 

(b) Using a 4-to-1 multiplexer

Figure 4.11. The circuits synthesized in Example 4.5.

$$f = w_1 w_2 + w_1 w_3 + w_2 w_3$$

Shannon's expansion:

$$\begin{aligned} f &= w_1' (w_2 w_3) + w_1 (w_2 + w_3 + w_2 w_3) \\ &= w_1' (w_2 w_3) + w_1 (w_2 + w_3) \end{aligned}$$

Let $g = w_2 w_3$ and $h = w_2 + w_3$.

Expanding both g and h using w_2 gives:

$$g = w_2' (0) + w_2 (w_3)$$

$$h = w_2' (w_3) + w_2 (1)$$

 


Figure 4.12. A 3-input majority function.