

BEE 271 Digital circuits and systems

Spring 2017

Lecture 8: Multiplexers and Shannon's expansion


Nicole Hamilton

<https://faculty.washington.edu/kd1uj>


Topics

1. Hazards
2. Multiplexers
3. Shannon's expansion


A circuit with a hazard

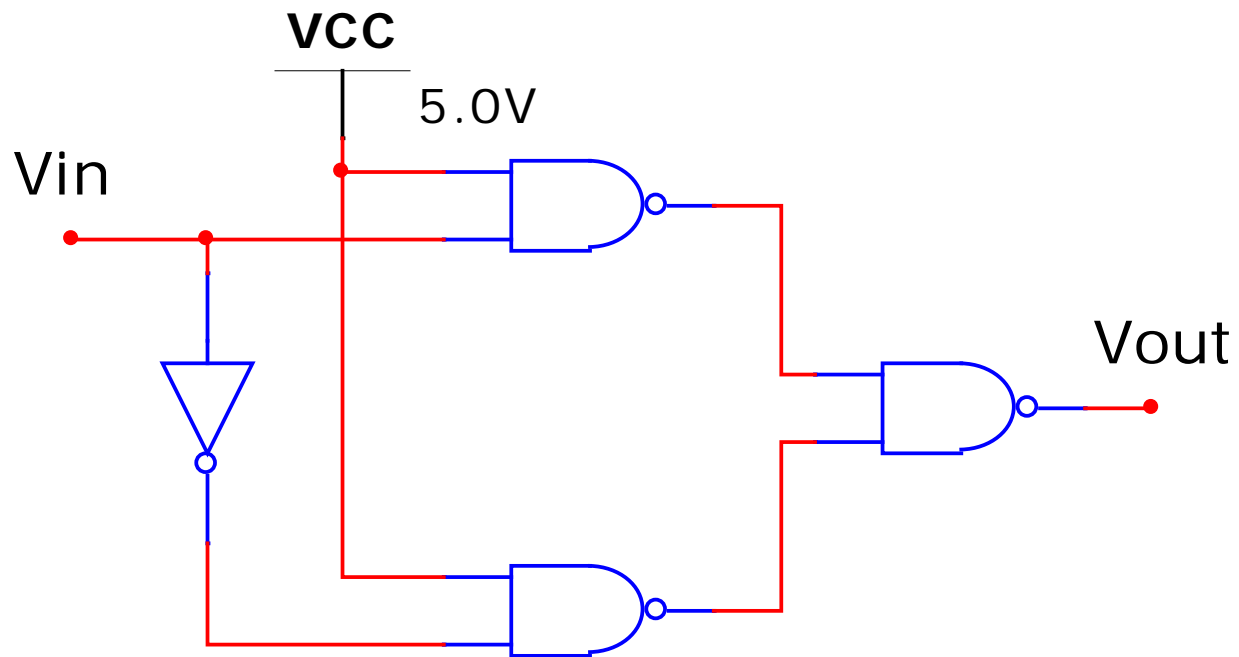

If $V_{in} = 0$, $V_{out} = 1$

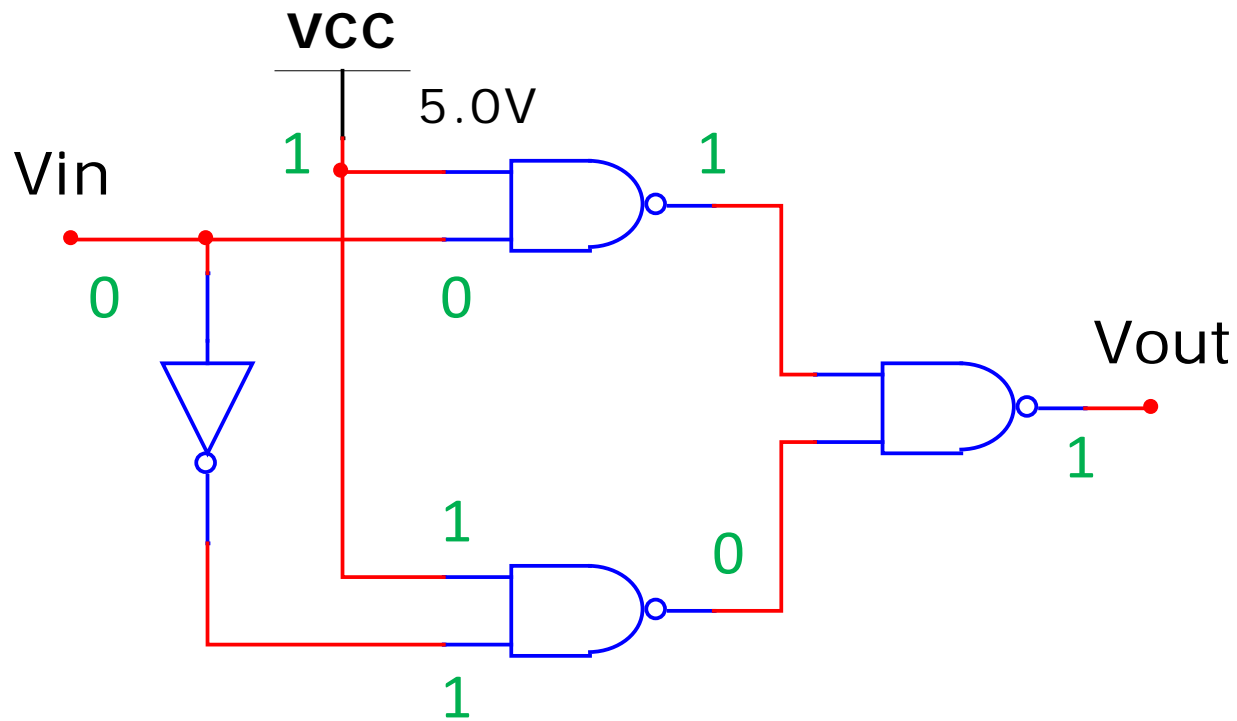

If $V_{in} = 1$, $V_{out} = 1$ (same)

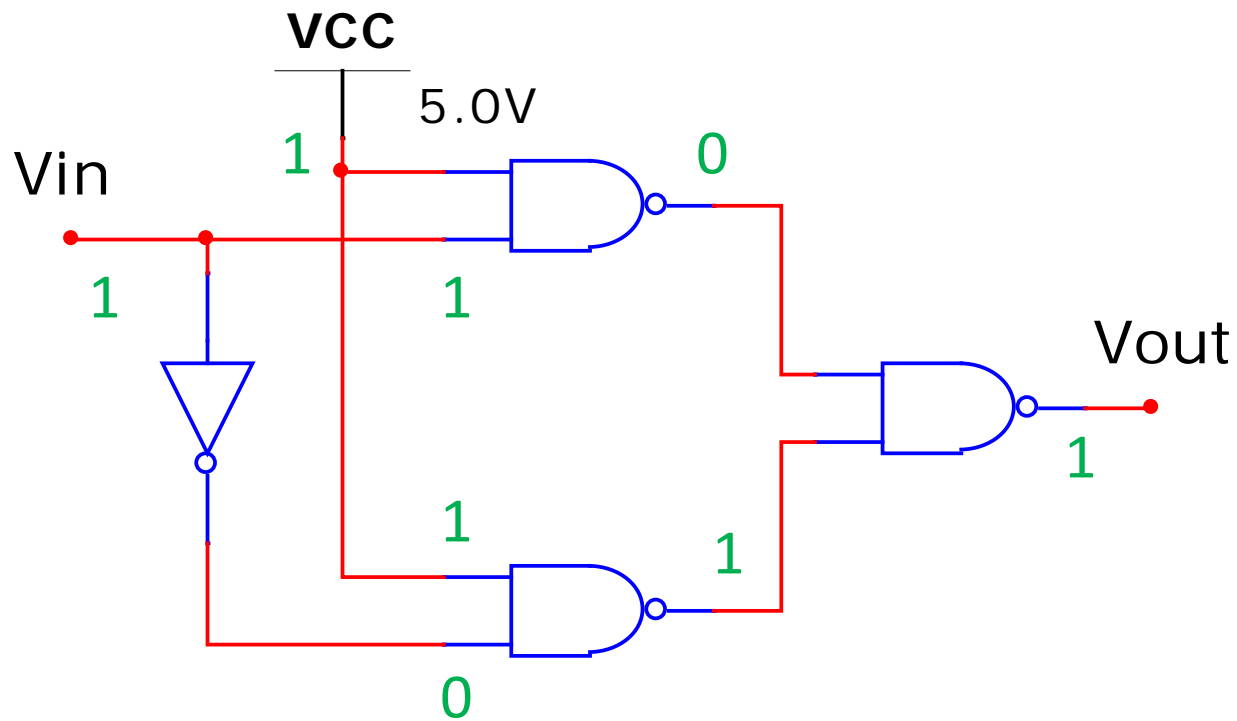

Tek Run

Trig'd






1 2.00 V 2 2.00 V 400ns 2.50GS/s 1 \int
1 \rightarrow 0.00000 s 10k points 2.80 V

	Value	Mean	Min	Max	Std Dev
1 Frequency	1.000MHz	1.000M	999.6k	1.000M	188.2
2 Min	-160mV	-146m	-320m	-80.0m	56.0m
2 Max	5.52 V	5.51	5.44	5.60	35.8m

20 Jun 2015
14:31:16

From homework 2

  

 


```
module Mux2To1wHazard(
    input  s, a, b,
    output f );
```

```
    wire g, h, k;
    not  ( k, s );
    and  ( g, k, a ),
        ( h, s, b );
    or   ( f, g, h );
```


```
endmodule
```

A circuit with a hazard

 


		a b				
		00	01	11	10	
s	0	0	0	1	1	$g = a s'$
	1	0	1	1	0	$h = b s$

 The hazard happens because we're switching between implicants that can never be assumed to have exactly identical path delays.



		a b				
		00	01	11	10	
s	0	0	0	1	1	$g = a s'$
	1	0	1	1	0	$h = b s$

 
It's called a *static one hazard* because we expect the output to remain 1 if a and b are both 1 and it doesn't.



		a b			
		00	01	11	10
s	0	0	0	1	1
	1	0	1	1	0

$h = b s$ $j = a b$ $g = a s'$

 We can eliminate the hazard by adding one more term so that if a and b are both 1, $f = 1$ no matter what the value of s .




```

module Mux2To1HazardFree(
    input  x1, x2, s,
    output f );

    wire g, h, j, k;
    not  ( k, s );
    and  ( g, k, x1 ),
        ( h, s, x2 ),
        ( j, x1, x2 );
    or   ( f, g, h, j );

endmodule

```

 

```

module Mux2To1B(
    input  x1, x2, s,
    output f );

    assign f = s ? x2 : x1;

endmodule

```

```


module Mux2To1C(
    input  x1, x2, s,
    output f );

    assign f = ~s & x1 | s & x2;

endmodule

```

 The Verilog compiler will automatically add the extra gate to make continuous assignments and behavioral descriptions hazard-free.



```


module Mux2To1D(
    input x1, x2, s,
    output reg f );

    always @( * )
        if ( s )
            f = x2;
        else
            f = x1;

endmodule

```

 The Verilog compiler will automatically add the extra gate to make continuous assignments and behavioral descriptions hazard-free.



		a b				
		00	01	11	10	
s	0	0	0	1	1	$g = a s'$
	1	0	1	1	0	$h = b s$

A *static one hazard* happens because you're collecting 1's for an SOP solution.

$$f = (s + a)(s' + b)$$

		a b		$s + a$	
		00	01	11	10
s	0	0	0	1	1
	1	0	1	1	0

$s' + b$

A *static zero hazard* happens you're collecting 0's for a POS solution. If a and b are both 0, it will glitch to 1 when switches to the slower implicant.

$$f = (s + a)(s' + b)(a + b)$$


		a b		$s + a$	
		00	01	11	10
s	0	0	0	1	1
	1	0	1	1	0
		$a + b$			$s' + b$

To fix a *static zero hazard*, we add back the extra POS term to ensure that if both a and $b = 0$, the output will remain 0.

multiplexers and decoders

- A *multiplexer* is a many-to-one function, selecting from a set of inputs (which could be vectors).
- An *encoder* or *decoder* translates from one encoding to another.
 1. Select highest priority.
 2. 4-bit binary to 1-of-16 select.
 3. 4-bit binary to 7-segment display.


The Multiplexer

 

Selects a or b based on s, *multiplexing* these signals onto the output f.


Multiplexer

 1. An element that selects data from one of many input lines and directs it to a single output line
2. Input: 2^N input lines and N selection lines
3. Output: The data from *one* selected input line
4. Multiplexer often abbreviated as MUX




```
module Mux2To1A(  
    input s, a, b,  
    output f );  
  
    wire g, h, k;  
    not ( k, s );  
    and ( g, k, a ),  
        ( h, s, b );  
    or  ( f, g, h );  
  
endmodule
```

Structural code for a multiplexer.

 


```
module Mux2To1D(  
    input s, a, b,  
    output f );  
  
    assign f = ~s & a | s & b;  
  
endmodule
```

Continuous assignment.

 

```
module Mux2To1F(  
    input s, a, b,  
    output reg f );  
  
    always @( s, a, b )  
        if ( s )  
            f = b;  
        else  
            f = a;  
  
endmodule
```


Behavioral description of a multiplexer.

 

Schematic symbol

s_1	s_0	f
0	0	w_0
0	1	w_1
1	0	w_2
1	1	w_3

Truth table

 

Circuit

A 4-to-1 multiplexer.


 


Figure 4.3. Using 2-to-1 multiplexers to build a 4-to-1 multiplexer.
 
```
module Mux4to1A( input [ 0:3 ] x, input [ 1:0 ] s,  
                output f );  
  
    assign f = s == 0 ? x[ 0 ] :  
               s == 1 ? x[ 1 ] :  
               s == 2 ? x[ 2 ] : x[ 3 ];  
  
endmodule
```




A 4-to-1 multiplexer.

```
module Mux4to1B( input [ 0:3 ] x, input [ 1:0 ] s,  
                output f );
```

```
    assign f = s[ 1 ] ?
```

```
        s[ 0 ] ? x[ 3 ] : x[ 2 ] :  
        s[ 0 ] ? x[ 1 ] : x[ 0 ];
```

```
endmodule
```

 

A 4-to-1 multiplexer.


```

module Mux4to1C( input [ 0:3 ] x, input [ 1:0 ] s,
                 output reg f );

always @( * )
    if ( s == 0 )
        f = x[ 0 ];
    else
        if ( s == 1 )
            f = x[ 1 ];
        else
            if ( s == 2 )
                f = x[ 2 ];
            else
                f = x[ 3 ];

endmodule

```

 

A 4-to-1 multiplexer.


```

module Mux4to1D( input [ 0:3 ] x, input [ 1:0 ] s,
                 output reg f );

always @( * )
    case ( s )
        0: f = x[ 0 ];
        1: f = x[ 1 ];
        2: f = x[ 2 ];
        3: f = x[ 3 ];
    endcase

endmodule

```

 

A 4-to-1 multiplexer.

```
module Mux4to1E( input [ 0:3 ] x, input [ 1:0 ] s,  
                output f );
```


```
    wire a, b;
```

```
    Mux2to1A ma ( x[ 0 ], x[ 1 ], s[ 0 ], a );
```

```
    Mux2to1A mb ( x[ 2 ], x[ 3 ], s[ 0 ], b );
```


```
    Mux2to1A mf ( a,      b,      s[ 1 ], f );
```

```
endmodule
```

 


A 4-to-1 multiplexer.

 
```
module Mux4to1F( input [ 0:3 ] x, input [ 1:0 ] s,  
                output f );  
  
    assign f = x[ s ];  
  
endmodule
```




A 4-to-1 multiplexer.

 

An 8-to-1 multiplexer.

 

A 16-to-1 multiplexer.

 

A 16-to-1 multiplexer built from 4-to-1 multiplexers.

```

module Mux16to1A( input [ 0:15 ] w,
                  input [ 3:0 ] s, output f );

    wire [ 0:3 ] m;

    Mux4to1 m1 ( w[ 0:3 ] , s[ 1:0 ] , m[ 0 ] );
    Mux4to1 m2 ( w[ 4:7 ] , s[ 1:0 ] , m[ 1 ] );
    Mux4to1 m3 ( w[ 8:11 ] , s[ 1:0 ] , m[ 2 ] );
    Mux4to1 m4 ( w[ 12:15 ] , s[ 1:0 ] , m[ 3 ] );
    Mux4to1 m5 ( m[ 0:3 ] , s[ 3:2 ] , f );

endmodule

```

A16-to-1 multiplexer.

```
module Mux16to1B( input [ 0:15 ] w,  
                 input [ 3:0 ] s, output reg f );
```

```
    always @( * )  
        case ( s )  
            0: f = w[ 0 ];  
            1: f = w[ 1 ];  
            2: f = w[ 2 ];  
            3: f = w[ 3 ];  
            4: f = w[ 4 ];  
            5: f = w[ 5 ];  
            6: f = w[ 6 ];  
            7: f = w[ 7 ];  
            8: f = w[ 8 ];  
            9: f = w[ 9 ];  
            10: f = w[ 10 ];  
            11: f = w[ 11 ];  
            12: f = w[ 12 ];  
            13: f = w[ 13 ];  
            14: f = w[ 14 ];  
            15: f = w[ 15 ];  
        endcase
```

```
endmodule
```

```
module Mux16to1C( input [ 0:15 ] w,  
                 input [ 3:0 ] s, output reg f );
```


```
    always @( * )  
    begin  
        if ( s == 0 ) f = w[ 0 ];  
        if ( s == 1 ) f = w[ 1 ];  
        if ( s == 2 ) f = w[ 2 ];  
        if ( s == 3 ) f = w[ 3 ];  
        if ( s == 4 ) f = w[ 4 ];  
        if ( s == 5 ) f = w[ 5 ];  
        if ( s == 6 ) f = w[ 6 ];  
        if ( s == 7 ) f = w[ 7 ];  
        if ( s == 8 ) f = w[ 8 ];  
        if ( s == 9 ) f = w[ 9 ];  
        if ( s == 10 ) f = w[ 10 ];  
        if ( s == 11 ) f = w[ 11 ];  
        if ( s == 12 ) f = w[ 12 ];  
        if ( s == 13 ) f = w[ 13 ];  
        if ( s == 14 ) f = w[ 14 ];  
        if ( s == 15 ) f = w[ 15 ];  
    end
```

```
endmodule
```


```
module Mux16to1D( input [ 0:15 ] w,  
                 input [ 3:0 ] s, output reg f );  
  
    always @( * )  
        begin  
            integer p;  
            for ( p = 0; p < 16; p = p + 1 )  
                if ( s == p )  
                    f = w[ p ];  
            end  
  
        endmodule
```

```
module Mux16to1E( input [ 0:15 ] w,  
                 input [ 3:0 ] s, output f );  
  
    assign f = w[ s ];  
  
endmodule
```

 Synthesis of logic functions using multiplexers




A 2 x 2 crossbar switch

 

Implementation using multiplexers

A practical application of multiplexers.

w_1	w_2	f
0	0	0
0	1	1
1	0	1
1	1	0

 


Implementation using a 4-to-1 multiplexer

w_1	w_2	f
0	0	0
0	1	1
1	0	1
1	1	0

w_1	f
0	w_2
1	w_2'


Modified truth table

 

Circuit

Synthesis of a logic function using multiplexers.


w_1	w_2	w_3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 

Synthesis of 3-input function using an 8-to-1 multiplexer.

$$f(a, b, c, d) = \sum m(5, 7, 8, 9, 10, 11, 12, 13, 14)$$


		cd			
		00	01	11	10
ab	00				
	01		1	1	
	11	1	1		1
	10	1	1	1	1

 

w_1	w_2	w_3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

w_1	w_2	f
0	0	0
0	1	w_3
1	0	w_3
1	1	1

Modified truth table

 

Circuit


A 3-input majority function using a 4-to-1 multiplexer.

w_1	w_2	w_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$w_2 \wedge w_3$

$(w_2 \wedge w_3)'$

Truth table

 


Circuit

A 3-input XOR implemented with 2-to-1 multiplexers.

w_1	w_2	w_3	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

} w_3
 } w_3'
 } w_3'
 } w_3'
 } w_3

Truth table

 

Circuit

A 3-input XOR function implemented with a 4-to-1 multiplexer.


Shannon's expansion theorem

Any Boolean function $f(w_1, w_2, \dots, w_n)$ can be written in the form:

$$f(w_1, w_2, \dots, w_n) = w_1' f(0, w_2, \dots, w_n) + w_1 f(1, w_2, \dots, w_n)$$

$f(0, w_2, \dots, w_n)$ is a *cofactor* of f with respect to w_1' , written $f_{w_1'}$

 $f(1, w_2, \dots, w_n)$ is a *cofactor* of f with respect to w_1 , written f_{w_1}




(a) Shannon's expansion of the function f .

Figure 4.10. The three-input majority function implemented using a 2-to-1 multiplexer.

w_1	w_2	w_3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

w_1	f
0	$w_2 w_3$
1	$w_2 + w_3$

Truth table

 

Circuit

$$f = w_1' w_3' + w_1 w_2 + w_1 w_3$$

Shannon's expansion for a 2-in mux:

$$f = w_1' f_{w_1'} + w_1 f_{w_1}$$

$$= w_1' (w_3') + w_1 (w_2 + w_3)$$


For a 4-in mux, expand again:

$$f = w_1' w_2' f_{w_1' w_2'} + w_1' w_2 f_{w_1' w_2}$$


$$+ w_1 w_2' f_{w_1 w_2'} + w_1 w_2 f_{w_1 w_2}$$

$$= w_1' w_2' (w_3') + w_1' w_2 (w_3')$$

$$+ w_1 w_2' (w_3) + w_1 w_2 (1)$$

 

(a) Using a 2-to-1 multiplexer

 

(b) Using a 4-to-1 multiplexer

Figure 4.11. The circuits synthesized in Example 4.5.

$$f = w_1 w_2 + w_1 w_3 + w_2 w_3$$

Shannon's expansion:

$$f = w_1' (w_2 w_3) + w_1 (w_2 + w_3 + w_2 w_3)$$

$$= w_1' (w_2 w_3) + w_1 (w_2 + w_3)$$

Let $g = w_2 w_3$ and $h = w_2 + w_3$.

Expanding both g and h using w_2 gives:

$$g = w_2' (0) + w_2 (w_3)$$

$$h = w_2' (w_3) + w_2 (1)$$

 


Figure 4.12. A 3-input majority function.

Decoders in Verilog

Select one of many outputs
or transform data.

```

module Decode2to4A( input [ 1:0 ] s, input enable,
                    output reg [ 0:3 ] f );

always @( * )
    if ( enable )
        case ( s )
            0: f = 4'b1000;
            1: f = 4'b0100;
            2: f = 4'b0010;
            3: f = 4'b0001;
        endcase
    else
        f = 4'b0000;

endmodule

```

A 2-to-4 binary decoder.

```

module Decode2to4B( input [ 1:0 ] s, input enable,
                   output reg [ 0:3 ] f );

always @( * )
    case ( { enable, s } )
        3'b100: f = 4'b1000;
        3'b101: f = 4'b0100;
        3'b110: f = 4'b0010;
        3'b111: f = 4'b0001;
        default: f = 4'b0000;
    endcase

endmodule

```

A 2-to-4 binary decoder.

```

module Decode2to4C( input [ 1:0 ] s, input enable,
                   output reg [ 0:3 ] f );

always @( * )
    case ( { enable, s } )
        3'b0xx: f = 4'b0000;
        3'b100: f = 4'b1000;
        3'b101: f = 4'b0100;
        3'b110: f = 4'b0010;
        3'b111: f = 4'b0001;
    endcase

endmodule

```

A 2-to-4 binary decoder.

```

module Decode4to16A( input [ 3:0 ] s, input enable,
                    output reg [ 0:15 ] f );

    wire [ 0:3 ] m;

    Decode2to4 d1( s[ 3:2 ], enable, m[ 0:3 ] );
    Decode2to4 d2( s[ 1:0 ], m[ 0 ], f[ 0:3 ] );
    Decode2to4 d3( s[ 1:0 ], m[ 1 ], f[ 4:7 ] );
    Decode2to4 d4( s[ 1:0 ], m[ 2 ], f[ 8:11 ] );
    Decode2to4 d5( s[ 1:0 ], m[ 3 ], f[ 12:15 ] );

endmodule

```

A 4-to-16 binary decoder.


```
module Decode4to16B(input [ 3:0 ] s, input enable,  
    output reg [ 0:15 ] f );  
  
    assign f = enable ? 1 << s : 0;  
  
endmodule
```

A 4-to-16 binary decoder.